 


Adders, multiplexers, latches, flip-flops



Overview

- **Combinatorial circuits**
 - Build up a **toolbox of useful circuits**
 - Adder, multiplexer, demultiplexer
- **Sequential circuits**
 - **Latches** and **flip-flops**
 - Basis for computer **memory**

Building an adder

- Goal: $x + y = z$ for 4-bit integers
 - Input: $x = x_3x_2x_1x_0$
 - Input: $y = y_3y_2y_1y_0$
 - Input: c_0 (carry-in to first column)
 - Output: $z = z_3z_2z_1z_0$
 - Output: c_4 (carry-out last column)

				c_0	
	x_3	x_2	x_1	x_0	
+	y_3	y_2	y_1	y_0	
	c_4	z_3	z_2	z_1	z_0

Building an adder

- Goal: $x + y = z$ for 4-bit integers
- First attempt:
 - Build a truth table
 - 9 input variables to 5 output variables

	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
c_4	z_3	z_2	z_1	z_0

c_0	x_3	x_2	x_1	x_0	y_3	y_2	y_1	y_0	c_4	z_3	z_2	z_1	z_0
0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	0	0	0	1	1	0	0	0	1	1
.
1	1	1	1	1	1	1	1	1	1	1	1	1	1

Divide and conquer!

- Let's figure out **one bit-at-a-time**
- **Input:**
 - 1 bit from x
 - 1 bit from y
 - 1 bit carry-in
- **Output:**
 - 1 bit for sum
 - 1 bit for carry-out

	c_3	c_2	c_1	c_0
	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
	c_4	z_3	z_2	z_1
		z_0		

Divide and conquer!

- Let's figure out **one bit-at-a-time**

- Input:**

- 1 bit from x
- 1 bit from y
- 1 bit carry-in

- Output:**

- 1 bit for sum
- 1 bit for carry-out

	C_3	C_2	C_1	C_0
	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
C_4	z_3	z_2	z_1	z_0

x_i	y_i	c_i	z_i
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Sum bit

x_i	y_i	c_i	c_{i+1}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Carry-out bit

Divide and conquer!

- Let's figure out **one bit-at-a-time**

- Input:**

- 1 bit from x
- 1 bit from y
- 1 bit carry-in

- Output:**

- 1 bit for sum
- 1 bit for carry-out

	c_3	c_2	c_1	c_0
	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
c_4	z_3	z_2	z_1	z_0

x_i	y_i	c_i	z_i	ODD
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Sum bit

x_i	y_i	c_i	c_{i+1}	MAJ
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Carry-out bit

ODD and MAJ


x_i	y_i	c_i	z_i	ODD
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Sum bit

$$z_i = x_i' y_i' c_i + x_i' y_i c_i' + x_i y_i' c_i' + x_i y_i c_i$$

$$= x_i \text{ XOR } y_i \text{ XOR } c_i$$

inputs

 


output

x_i	y_i	c_i	c_{i+1}	MAJ
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Carry-out bit

$$c_{i+1} = y c_i + x c_i + x y$$

output

 


inputs

Building a full adder

- Goal: $x + y = z$ for 4-bit integers




	x_3	x_2	x_1	x_0
+	y_3	y_2	y_1	y_0
c_4	z_3	z_2	z_1	z_0

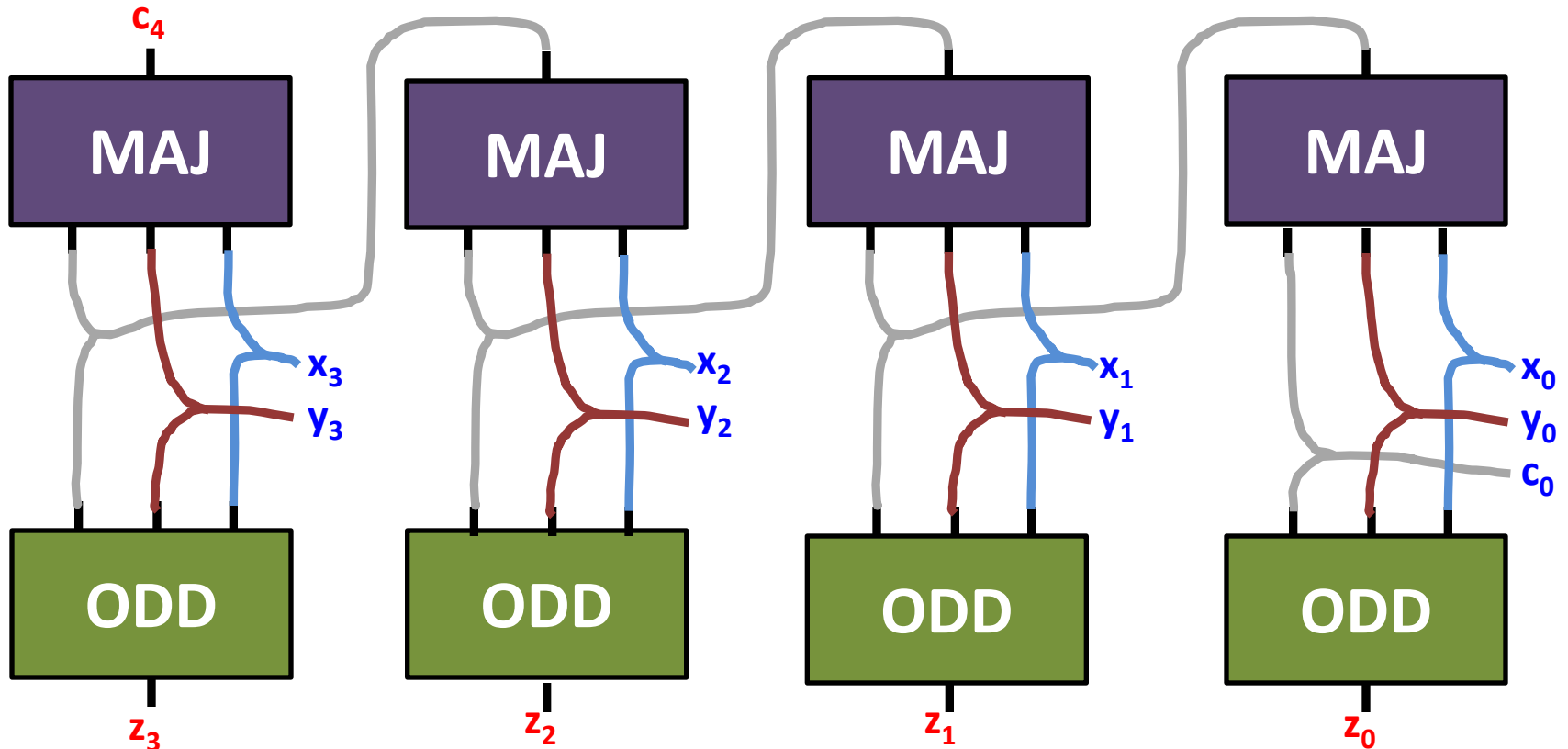

Multiplexer

- 2^n -to-1 multiplexer

 
 
 
- Copies selected input bit to output bit, controlled switch
- Input: n selection bits, 2^n input bits
- Output: 1 output bit



Demultiplexer

- 1-to- 2^n demultiplexer

 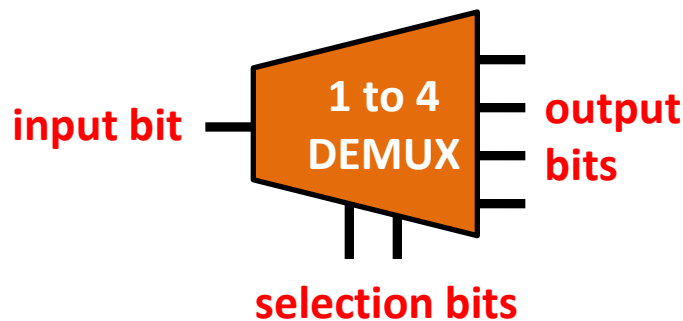 
- Copies single input bit to one of 2^n output bits
- Input: n selection bits, 1 input bits
- Output: 2^n output bits



Combinational vs. Sequential circuits


- **Combinational circuits**

 - Output **determined only by inputs**
- Can draw with signals going strictly **left-to-right**



- **Sequential circuits**

 - Output determined **by inputs and previous outputs**
- **Feedback loop!**




SR latch

- SR Latch


- Basic sequential circuit for **storing a bit**
- Input bit: **S = SET** (turn the bit on)
- Input bit: **R = RESET** (turn the bit off)

S (set)	R (reset)	Q(t)	Q(t+1)
0	0	x	x
0	1	x	0
1	0	x	1
1	1	x	not used

 
Excitation table for SR latch.
x = value (0 or 1) at time Q(t)




SR latch variants

 

SR latch
Set and reset on high signal

 

 
SR NOR latch
Set and reset on high signal



S'R' NAND latch
Set and reset on low signal


SR latch with enable

 - Often we want to **control when latching occurs**
- **Add enable line**
 - Must be high to SET / RESET



D latch with enable

 
- D latch (D for "data")
 - Eliminates invalid input: $S=R=1$
 - Whenever enable high, memorizes D bit



D (data)	E (enable)	Q(t)	Q(t+1)
0	0	x	x
0	1	x	0
1	0	x	x
1	1	x	1

Excitation table for D latch with enable.
x = value (0 or 1) at time Q(t)

Clock

 

- Clock


- Fundamental component of computers

- Synchronizes different circuit elements

- Regular on-off pulse

- Pulse less often than worst case internal propagation delay of any circuit


 
- 1 GHz clock = 1 billion pulses per second



Clocked D flip-flop

- D flip-flop

  - Hook the **enable line to a clock**
- Clocked latch = **flip-flop**
- State change has to wait for next clock cycle



D (data)	C (clock)	Q(t)	Q(t+1)
0	high	x	0
1	high	x	1

JK flip-flop

- JK flip-flop


- Refinement of SR flip-flop

- SET: $J=1, K=0$

- RESET: $J=0, K=1$

- TOGGLE: $J=1, K=1$ (flips the stored bit)


J	K	C (clock)	Q(t)	Q(t+1)
0	0	high	x	x
0	1	high	x	0
1	0	high	x	1
1	1	high	x	x'

 

T flip-flop

- T flip-flop “toggle”
 - Like JK but connect J and K together
 - LEAVE: $T=0$
 - **TOGGLE: $T=1$** (flips the stored bit)

T	C (clock)	Q(t)	Q(t+1)
0	high	x	x
1	high	x	x'

 

Summary

- Combinational circuits
 - How we compute things
 - Built from basic gates like {AND, OR, NOT}
 - Examples: MAJ, ODD, adder, (de)multiplexer
- Sequential circuits
 - How we remember things
 - Clock needed to synchronize things
 - Latches + clock = flip-flop
 - Examples: SR latch, D flip-flop, JK flip-flop, T flip-flop