

Due: **9/9/2013** at the beginning of lab

SHOW YOUR WORK


1 Prove the following logical theorems using Boolean algebra:

- a) $X (X' + Y) = XY$
- b) $X + XY = X$
- c) $XY + XY' = X$
- d) $(A+B)(A+B') = A$

2 Simplify the following expressions to a minimum expression

- a) $[(AB)' + C'D]'$
- b) $[A + B(C' + D)]'$
- c) $[(A + B') C]' (A + B)(C + A)'$

3 Find **F** and simplify:


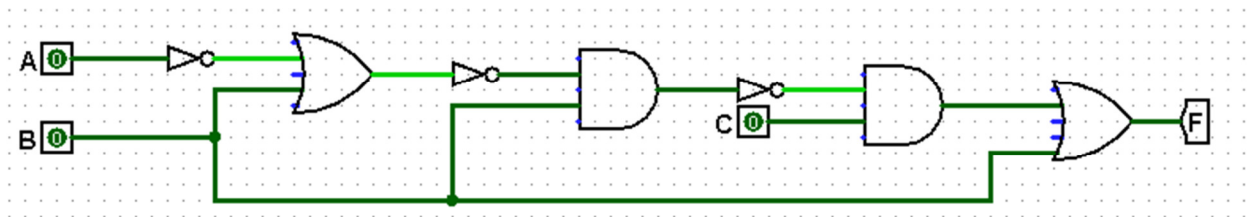


4 Draw a circuit that uses two OR-gates and two AND-gates to realize the following function:

$$F = (V + W + X)(V + X + Y)(V + Z)$$

Hint: when using the theorems wisely, it can be solved in 2 steps

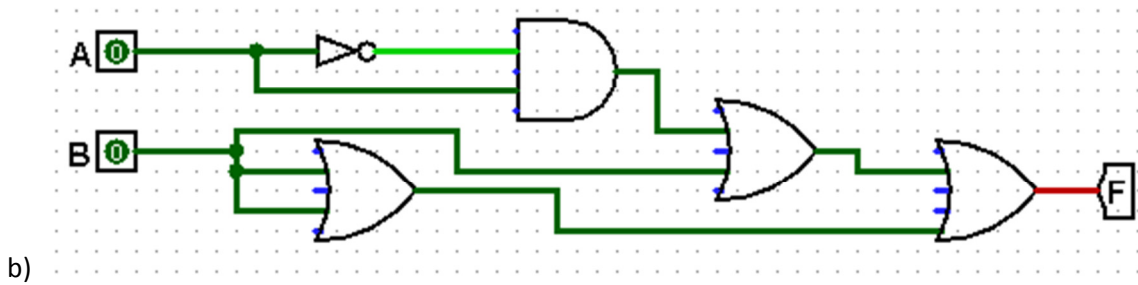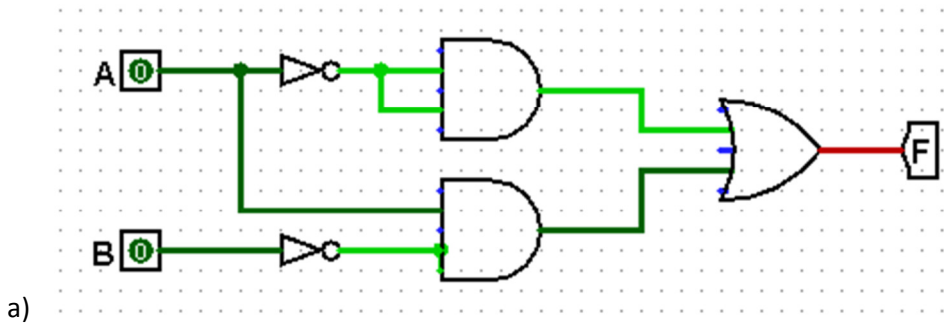5 For each of the following circuits, find the output and design a simpler circuit that has the same output:



6 Prove the following equations using truth tables:

a) $W'XY + WZ = (W' + Z)(W + XY)$

b) $(A + C)(AB + C') = AB + AC'$

7 Perform the following logical expressions:

<pre> 1 0 1 0 1 1 1 1 1 1 1 0 1 1 1 1 ----- </pre> <p>(AND)</p>	<pre> 1 0 1 0 1 1 1 1 1 1 1 0 1 1 1 1 ----- </pre> <p>(OR)</p>
<pre> 1 0 1 0 1 1 1 1 1 0 1 0 0 1 1 1 ----- </pre> <p>(OR)</p>	<pre> 0 0 1 1 1 1 0 1 1 1 1 0 1 0 1 1 ----- </pre> <p>(AND)</p>