 



Work must be done individually

Due: **10/23/2013** by **beginning of class**


1. Draw the Q-output signal when analyzing the SR-Latch inputs below: (Assume $Q=0$ @ $t=0$)



 
2. Draw the Q-output signal when analyzing the SR-Latch inputs below: (Assume $Q=1$ @ $t=0$)



 
3. Draw the Q-output signal when analyzing the D-Latch inputs below: (Assume $Q=1$ @ $t=0$)



 
4. Draw the Q-output signal when analyzing the T-FF inputs below: (Assume Positive Edge and Q value=1 @ $t=0$ is given)



 5. Draw the Q-output signal when analyzing the JK-FF inputs below: (Assume Positive Edge and $Q=0$ @ $t=0$)




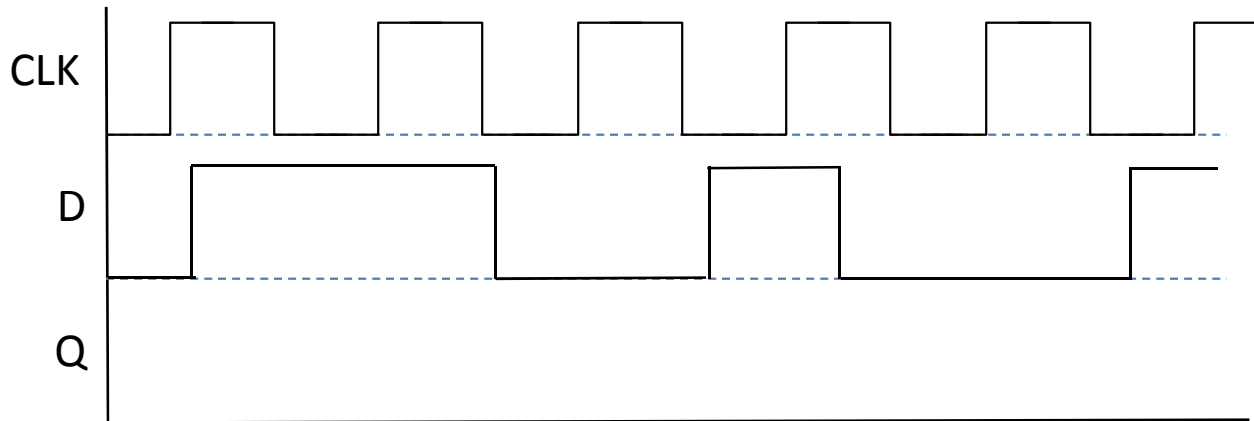6. Draw the Q-output signal when analyzing the D-FF inputs below: (Assume Negative Edge and $Q=0$ @ $t=0$)



 7. Draw the Q-output signals of each Flip-flop below to their corresponding signals, assume:

- D-FF and T-FF react to the negative edge
- JF-FF react to the positive edge
- $Q = (Q_D + Q_T) \text{ xor } Q_{JK}$ (Remember that combinational circuitry does not react to CLK)
- Assume $Q_D, Q_T, Q_{JK} = 0$ @ $t=0$



8. From the circuit below complete the timing diagram, assume positive edge and $Q_s=1$ at $t=0$

