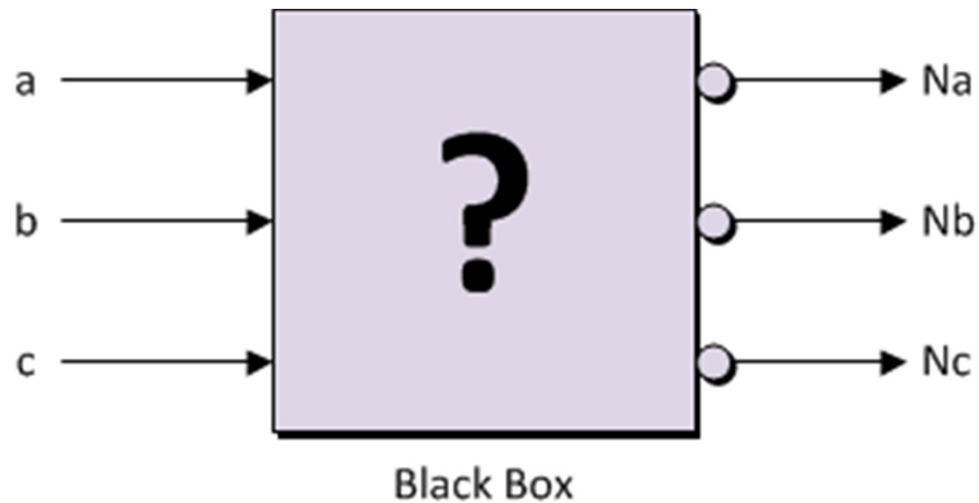


Carpe Gates!!!!... & Diem Data CSCI 255




http://img.deusm.com/programmableplanet/2012/06/246072/173837_783569.gif



Digital Gates

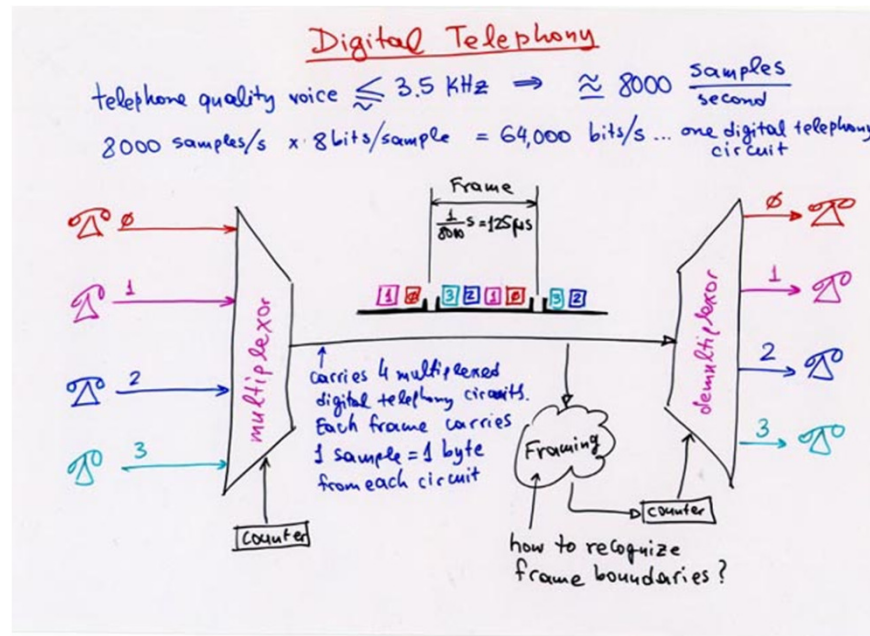
- Previous notes (and class), we have covered the BIG 3
 - AND, OR, NOT
- We will look in how to derive other digital gates
 - NOR,
 - NAND,
 - XOR,
 - MUXes,
 - Decoders....




http://www.csd.uoc.gr/~hy534/05a/s23_ts.html



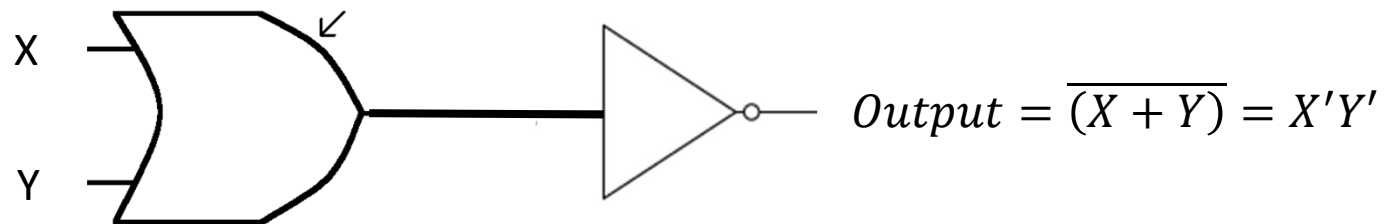- NOR Gate
- Gate representation of an OR-gate with a complemented output
- Gate diagram & Truth table:




INPUT 1 (X-value)	INPUT 2 (Y-value)	OUTPUT (x NOR y)
0	0	1
0	1	0
1	0	0
1	1	0

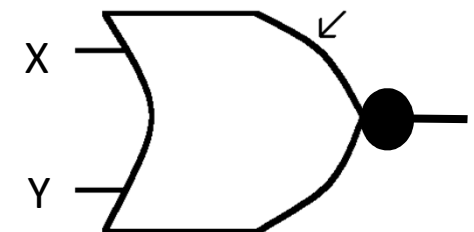


- NOR Gate(s) as:


NOT Gate

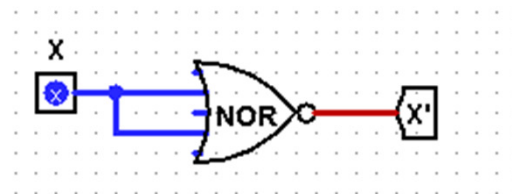


AND Gate

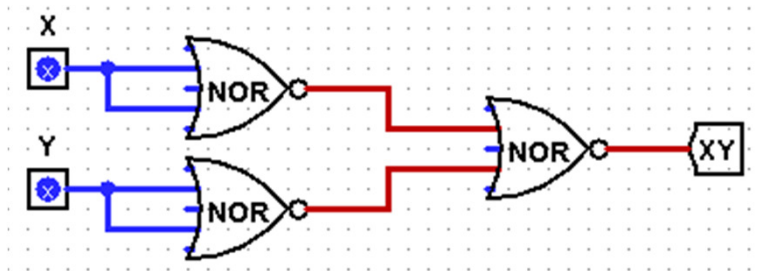


OR Gate

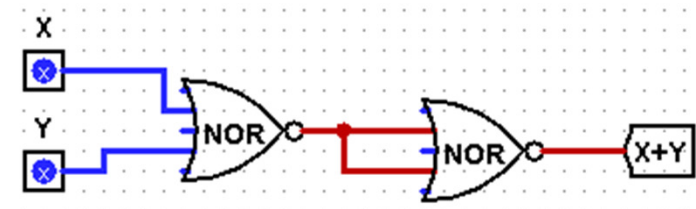

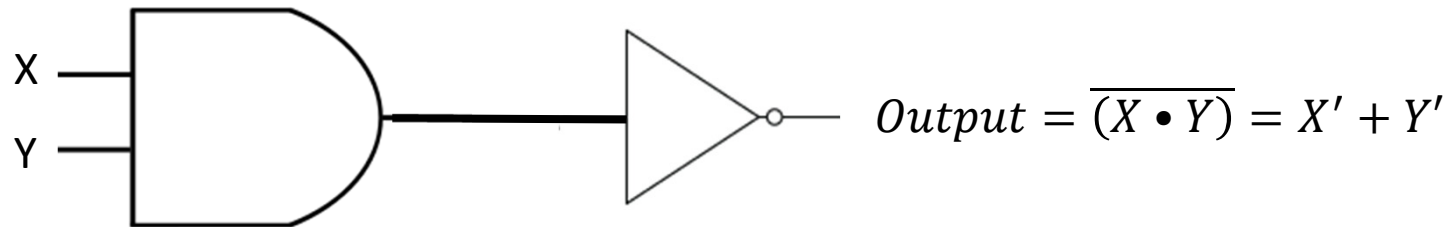- NAND Gate
- Gate representation of an AND-gate with a complemented output
- Gate diagram & Truth table:




INPUT 1 (X-value)	INPUT 2 (Y-value)	OUTPUT (x NAND y)
0	0	1
0	1	1
1	0	1
1	1	0

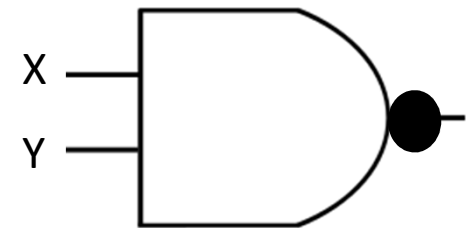


- NAND Gate(s) as:


NOT Gate

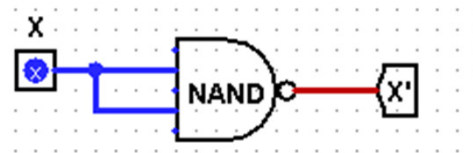


AND Gate

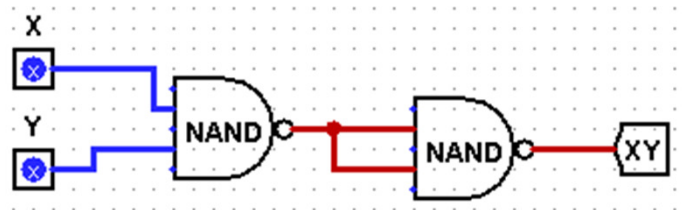

OR Gate

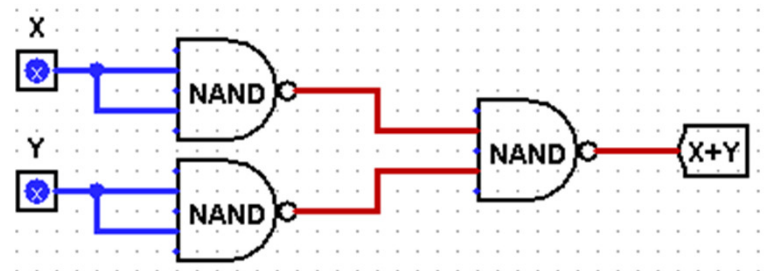


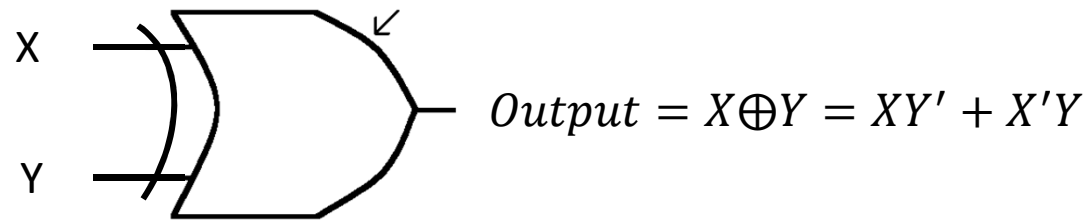- Exclusive-OR Gate (aka XOR)
- XOR is true when the inputs are exclusively different, false when the same
- Gate diagram:



INPUT 1 (X-value)	INPUT 2 (Y-value)	OUTPUT (x XOR y)
0	0	0
0	1	1
1	0	1
1	1	0

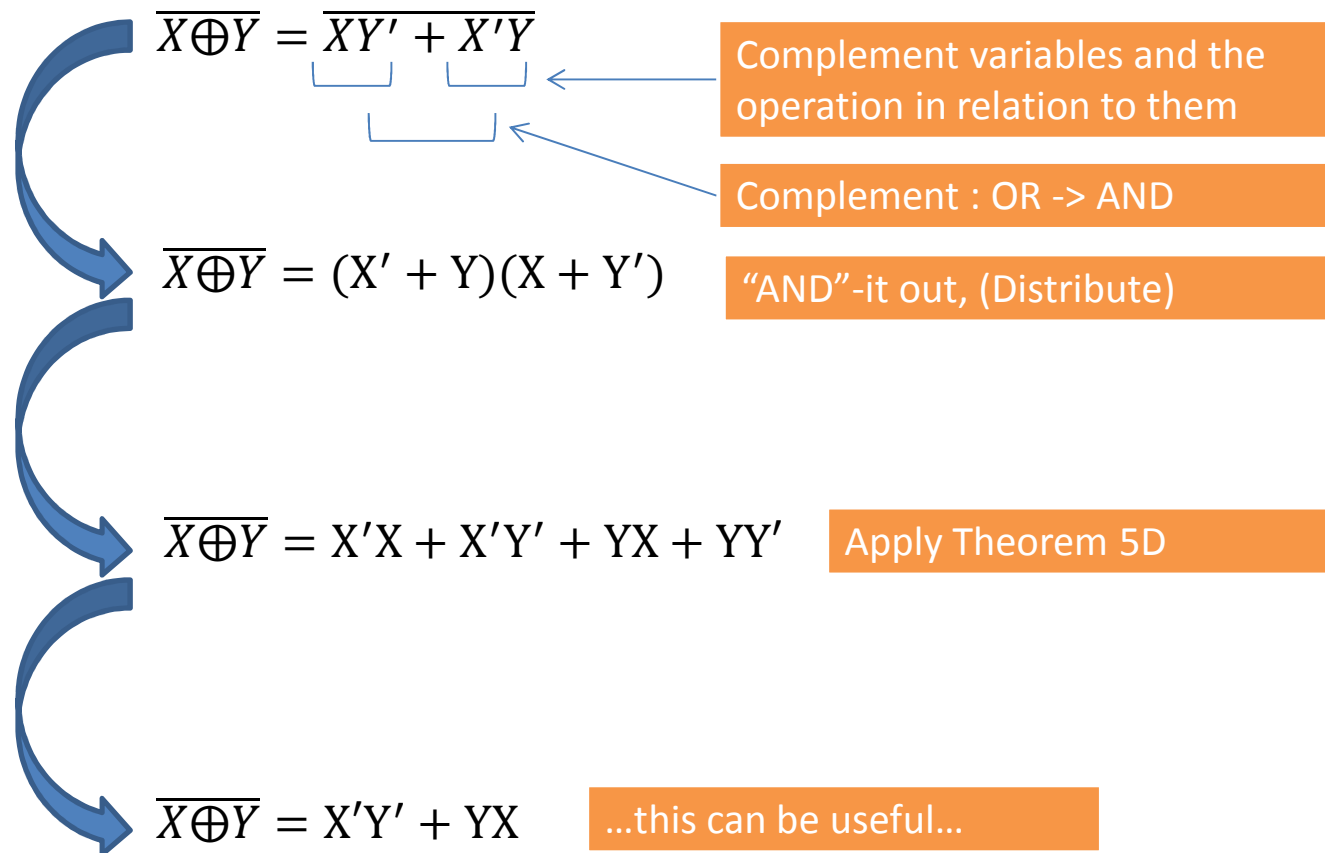
- What happens when applying DeMorgan's to the XOR???




- Multiplexers – (aka MUXes): *“Select the input you want” -- me again*
- MUXes come in different sizes, with three major components
 - Input lines
 - Single Output line
 - Selection lines
- The selection lines must satisfy:

$$\text{number of Input Lines} = 2^{\text{number of Selection Lines}}$$


- Simple 2-to-1 MUX:

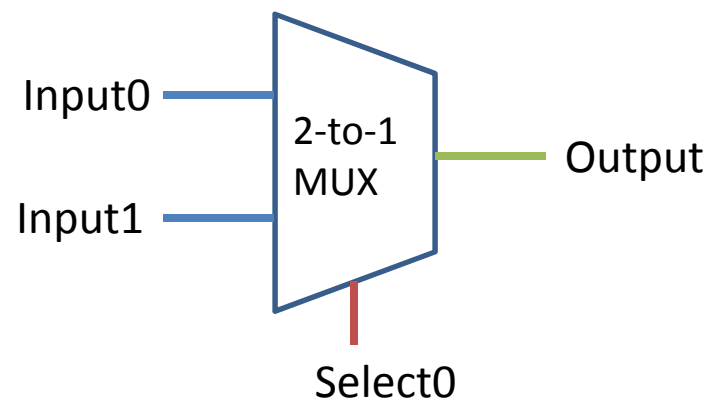

- How does it work??

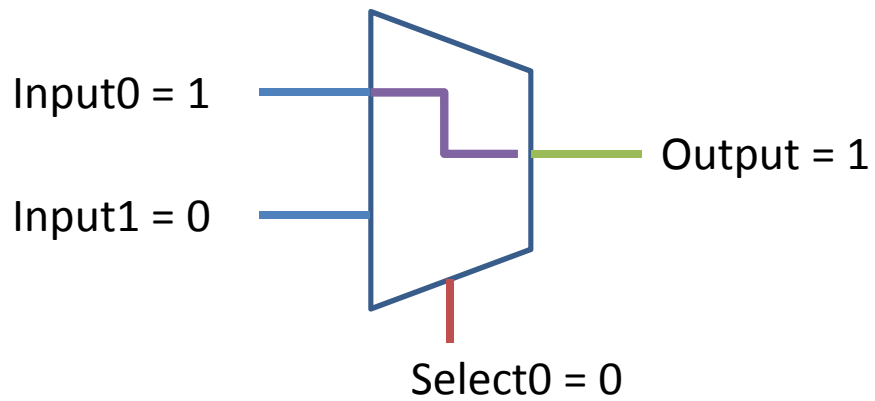

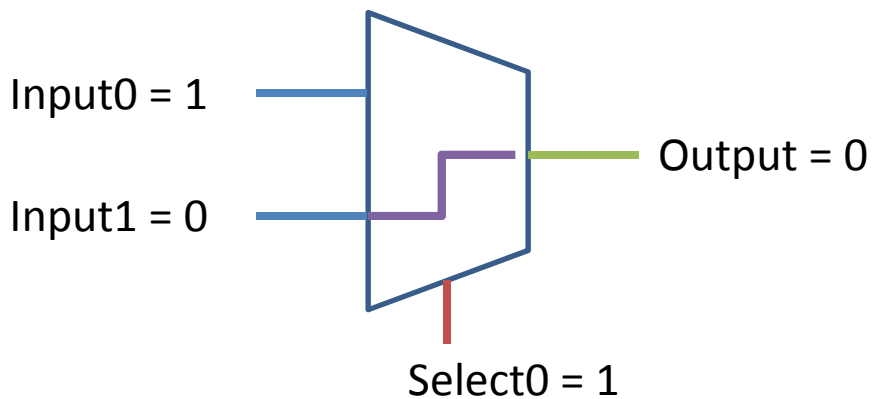
When Select line = 0; Value of Input0 will go through the Output line



When Select line = 1; Value of Input1 will go through the Output line



- 4-to-1 MUX:

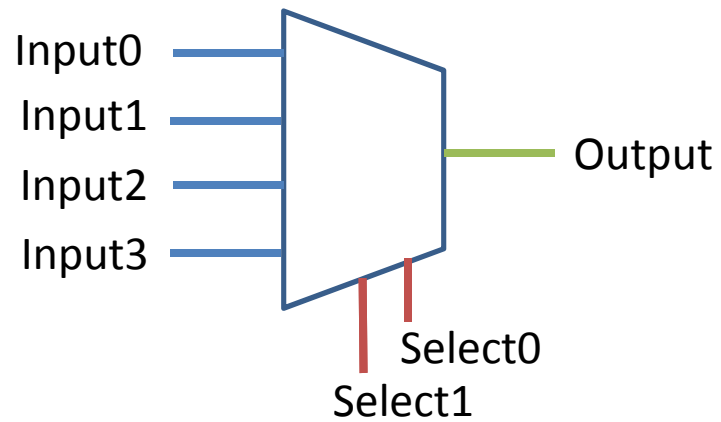


Select (Sel1:Sel0)	OUTPUT
00	Input0
01	Input1
10	Input2
11	Input3




- Demultiplexers – (aka Demuxes): *“Select the output you want” -- me again*
- Three major components
 - Input line
 - Output lines
 - Selection lines
- The selection lines must satisfy:

$$\text{number of Output Lines} = 2^{\text{number of Selection Lines}}$$


- Simple 1-to-2 Demux:

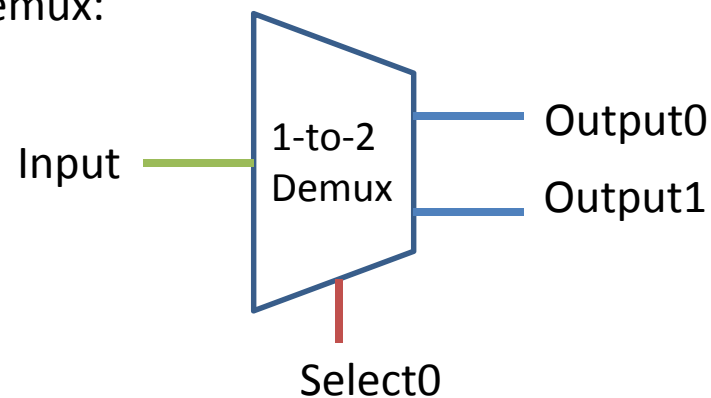

- How does it work??

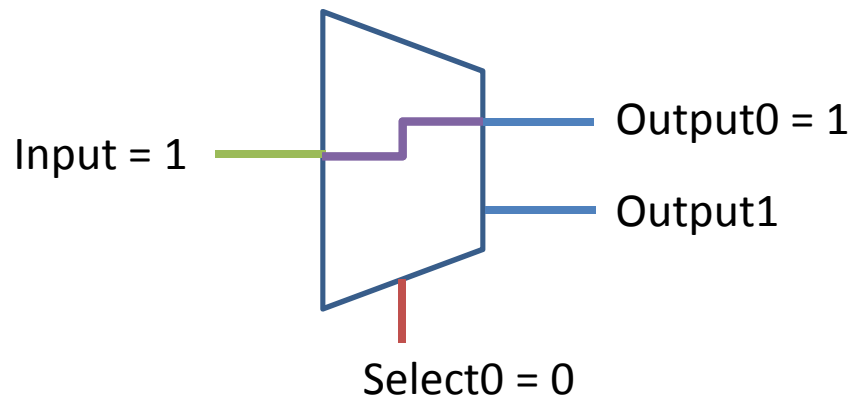

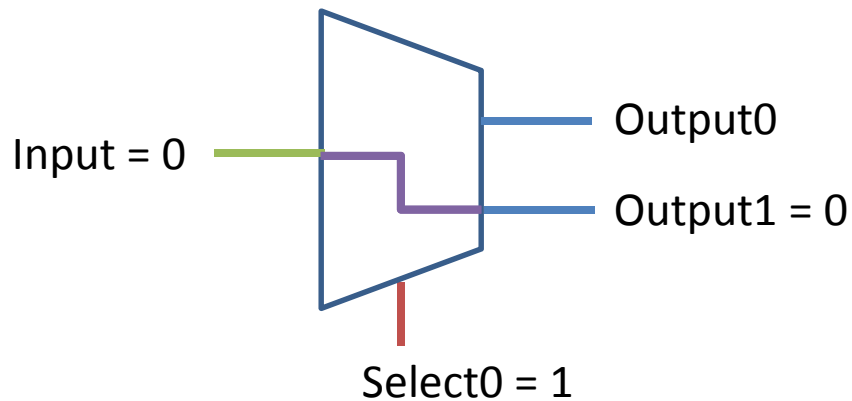
When Select line = 0; Value of Input will go through the Output0 line; other output lines do not have values



When Select line = 1; Value of Input will go through the Output1 line; other output lines do not have values



- 1-to-4 Demux:

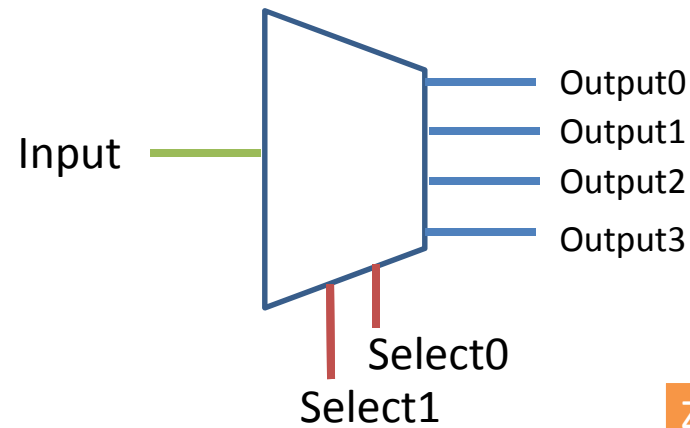

Z-value: High Impedance


Select (Sel1:Sel0)	OUTPUT0	OUTPUT1	OUTPUT2	OUTPUT3
00	Input	Z	Z	Z
01	Z	Input	Z	Z
10	Z	Z	Input	Z
11	Z	Z	Z	Input




- Decoder : *“Decode the incoming information in order to provide the whole message” -- me again*
- Decoders are mainly designed & utilized for RAM memory management
- Address & Data lines
- Decoders have a design that satisfies:

$$\text{number of Data Lines} = 2^{\text{number of Address Lines}}$$


- Simple 1-to-2 Decoder:

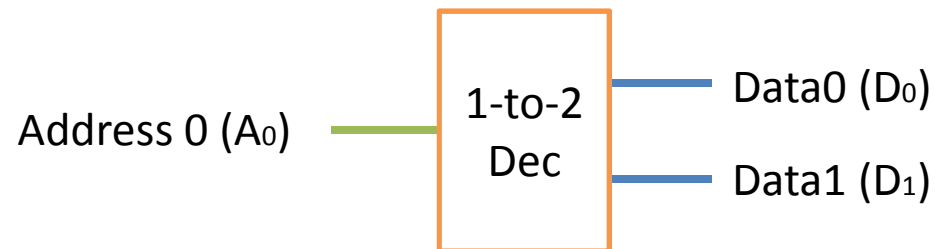

- How does it work??

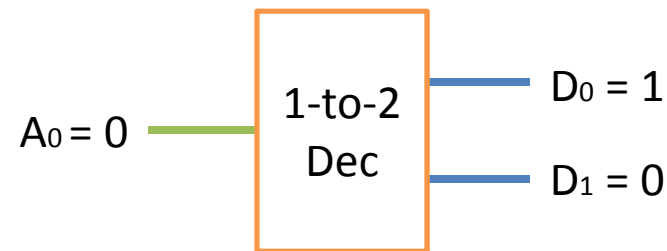

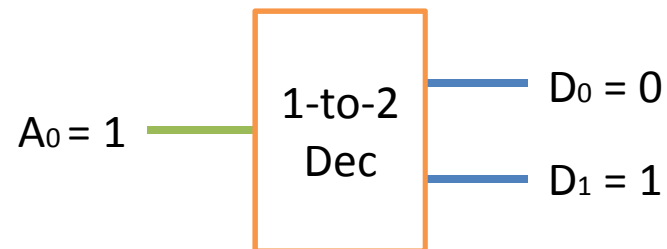
When address line = 0; First data line is true; while all other data lines are false



When address line = 1; Second data line is true; while all other data lines are false



- 2-to-4 Demux:

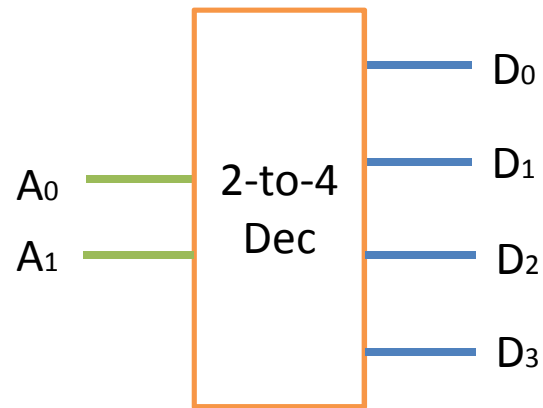


A_1	A_0	D_3	D_2	D_1	D_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0




- Encoder : *“Duh, the opposite of the decoder...” -- me again*
- Also, mainly designed & utilized for RAM memory management
- Address & Data lines
- Encoders have a design that satisfies:

$$\text{number of Address Lines} = 2^{\text{number of Data Lines}}$$


- Simple 2-to-1 Decoder:

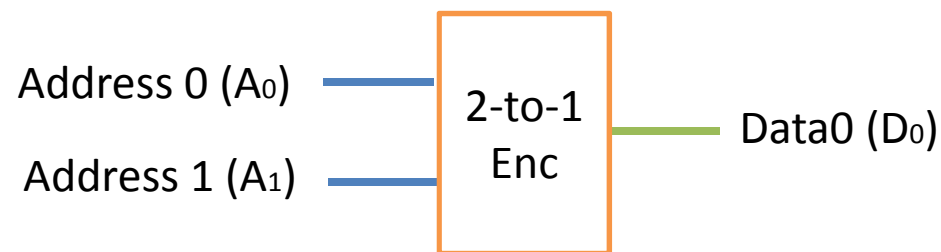

- How does it work??

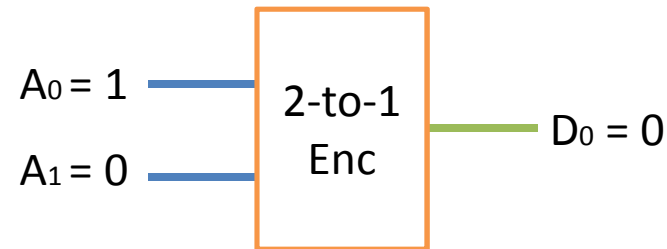

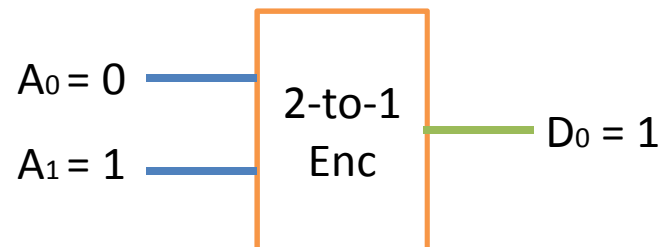
The data line value (zero) points to the address line which is true (A_0); other address lines are false



The data line value (one) points to the address line which is true (A_1); other address lines are false



- 2-to-4 Demux:

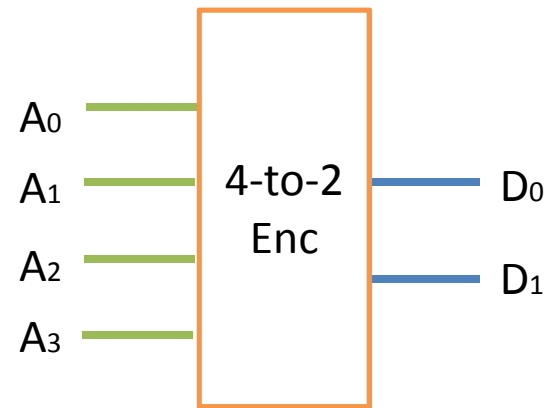

A ₃	A ₂	A ₁	A ₀	D ₁	D ₀
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1



Digital Gates

Gates OUT!!!!



<http://static4.businessinsider.com/image/517700336bb3f7394f000008-480/psy-bill-gates.jpg>

