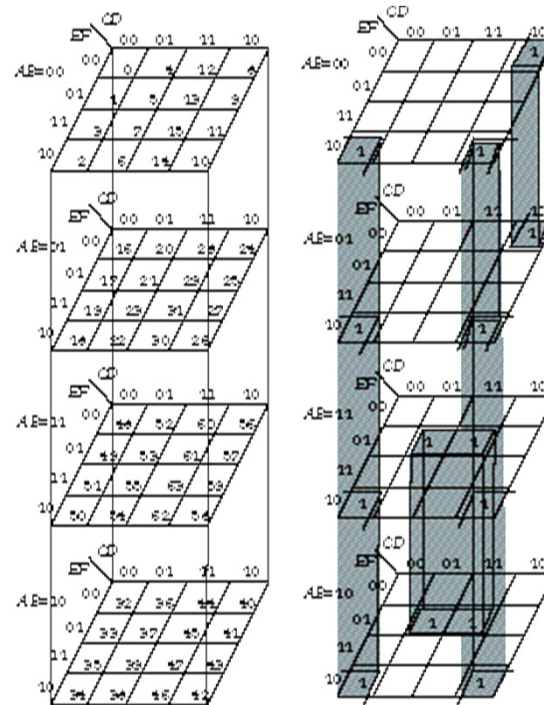


Trust me...its easier!!!

CSCI 255



(a) Six-variable K-map (b) Example

Figure 1.52 Six-variable K-map and example

<http://www2.elo.utfsm.cl/~lsb/elo211/aplicaciones/katz/chapter2/chapter02.doc3.html>



- K-Maps, short for: Karnaugh Maps
- Maurice Karnaugh from Bell Labs
- We all have learned to love this guys at some point
- Now that we have done plenty of Boolean, K-maps becomes a better way to reduce expressions
- Optimization of expression: better circuit designs



- K-maps: best way to explain them is to use an example.
- Ex: Random Truth Table

C	B	A	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

1 – Learn to setup the K-map

- We have three-inputs (A,B,C); therefore, we need a 3-variable K-Map
- We are trying to derive an optimized expression for output (OUT)
- All outcomes of the truth table must be mapped to the K-map




msb		lsb	
C	B	A	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

1 – Learn to setup the K-map (con't)

- The map looks like a matrix table
- Labeling ROWS & COLUMNS

 Usually you want to have the MSBits as rows & LSBits as columns...
Go to class and find out why




For bits C & B, the order of the bits are not in sequence. The difference between the each row is the 1-bit difference of change between C & B.



2 – How to read coordinates on K-map

C	B	A	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

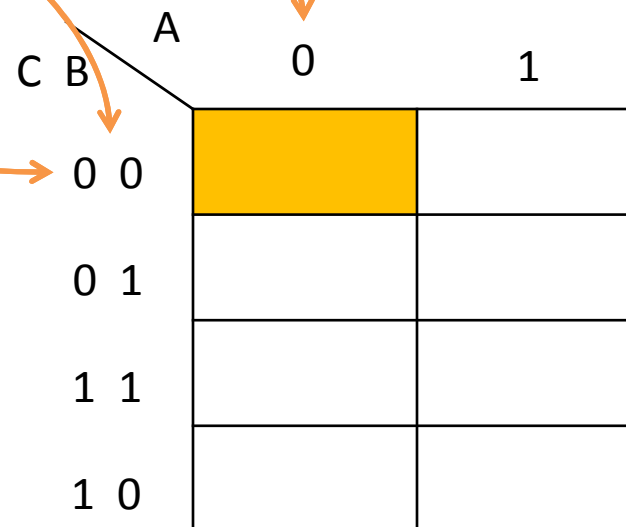- Each element on the map represents a row on the truth table



2 – How to read coordinates on K-map (con't)

C	B	A	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- Once coordinates have been identified, place output value to the element on the k-map

		A	
		0	1
C	B		
	0	0	1
	1		
	0		
	1		
	0		




2 – How to read coordinates on K-map (con't)

- Fill in the rest...

C	B	A	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


		A	
		0	1
C B	0 0	1	0
	0 1		
	1 1		
	1 0		

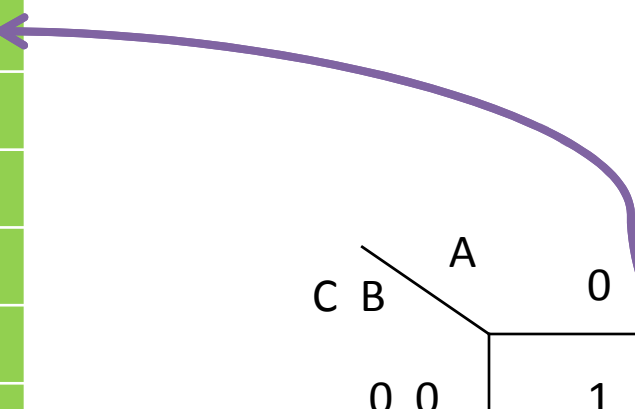

2 – How to read coordinates on K-map (con't)

C	B	A	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


- Fill in the rest...

 

2 – How to read coordinates on K-map (con't)

- Fill in the rest...

C	B	A	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 


2 – How to read coordinates on K-map (con't)

- Fill in the rest...

C	B	A	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

C B		A	
		0	1
0	0	1	0
0	1	0	1
1	1		
1	0	0	

 

2 – How to read coordinates on K-map (con't)

- Fill in the rest...

C	B	A	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

		A	
		0	1
C	B		
	0	0	1
0	1	0	1
1	1		
1	0	0	1



2 – How to read coordinates on K-map (con't)

- Fill in the rest...

C	B	A	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

		A	
		0	1
C	B		
	0	0	1
0	1	0	1
1	1	1	
1	0	0	1




2 – How to read coordinates on K-map (con't)

- Fill in the rest...


C	B	A	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

C B		A	
		0	1
0	0	1	0
0	1	0	1
1	1	1	1
1	0	0	1

 

3 – Grouping the ones:

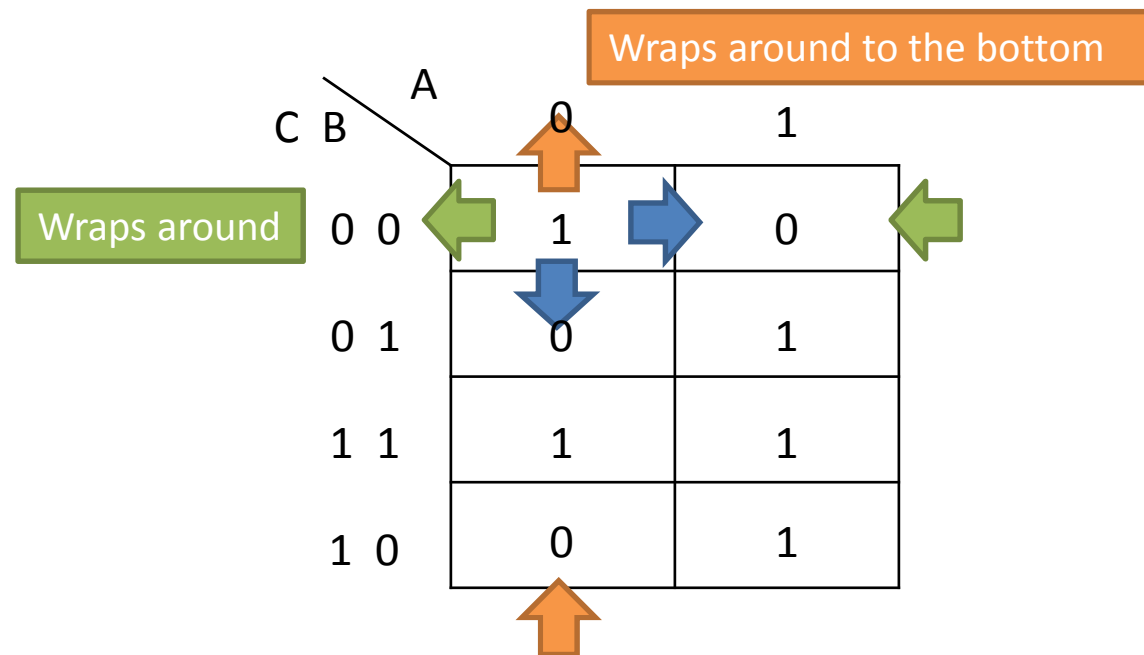
- Find the **maximum** group of **1s** on the map
- The size of the groups must be of \log_2
 - i.e: 1, 2, 4, 8, 16,...
- A **1** can only be grouped with neighboring **1s**, why? **ONE BIT OFFSET**
- The neighboring of a **1** can be found around all sides: up,down,left,right



3 – Grouping the ones (con't)

- For this first **1**, all neighbors are **0's**
- Therefore, the largest group of this **1** is one

		A	
		0	1
C	B	0	1
0	0	1	0
0	1	0	1
1	1	1	1
1	0	0	1

 


		A	
		0	1
C	B	0	1
0	0	1	0
0	1	0	1
1	1	1	1
1	0	0	1



3 – Grouping the ones (con't)

 - Move to another free **1**, check its neighbors, find max grouping




- In this grouping, a neighboring **1** exists to the right (or left...same 1).
- Maximum group is 2



3 – Grouping the ones (con't)

 - Move to another free **1**, check its neighbors, find max grouping




- A free **1** can use another **1** that is already part of another grouping
- This is part of maximizing the grouping → optimizing expression



3 – Grouping the ones (con't)

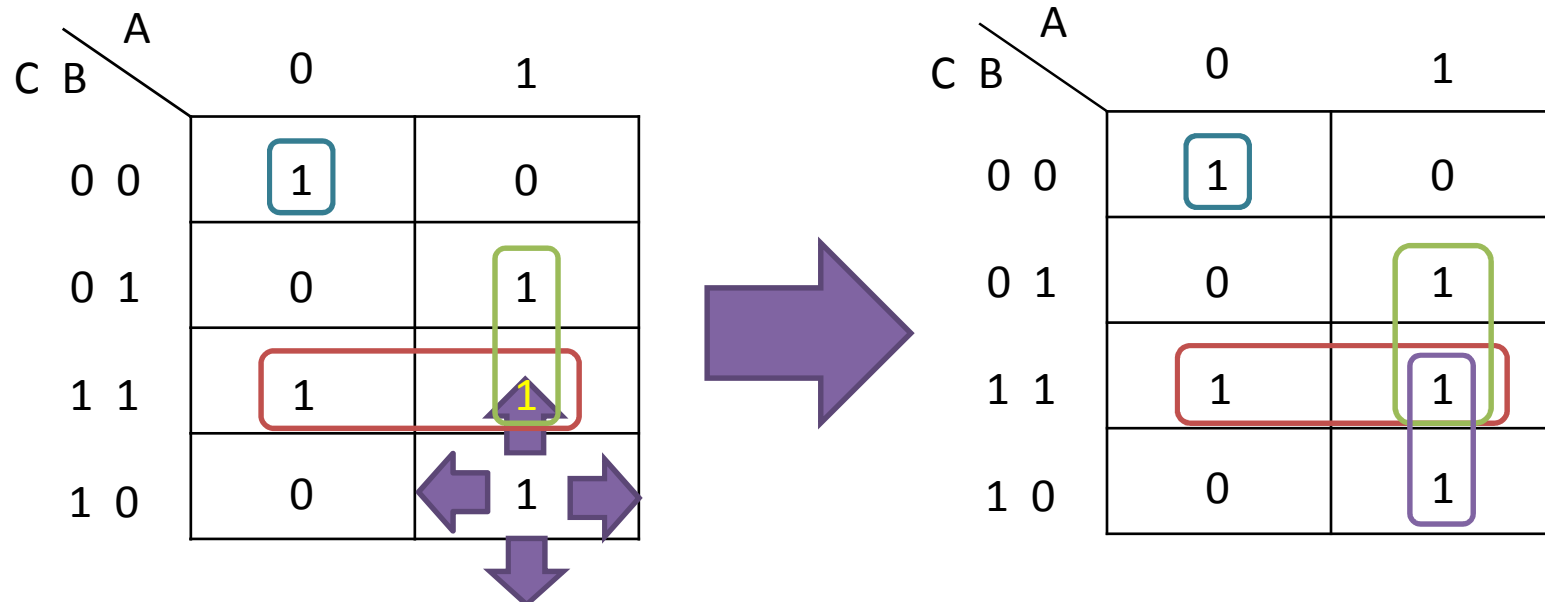- Move to another free 1, check its neighbors, find max grouping



- At this point, no more free 1s exists on the k-map -> got to stop!
- Four groups were form with the k-map



4 – Derive Expression from K-map

- Once all grouping are formed, need to derived **OUT**'s expression
- Each group represents a PRODUCT (AND) term of the input variables
- We derived the term of the 1st group:

		A	
		0	1
C	B		
	0	0	1
	1	0	1
	1	1	1
	0	1	

For this grouping, we observe:

- It consists of a single element
- Within this group:
 - $A=0, B=0 \text{ \& } C=0$
- Values of A,B,C remain constant
- Therefore, no need to cancel any of the input variables
- At the end, the term of this group is: **$A'B'C'$**
- They are complemented because of the values of A, B & C = 0



4 – Derive Expression from K-map (con't)

		A	
		0	1
C	B		
	0 0	1	0
	0 1	0	1
	1 1	1	1
1 0	0	1	

For this group, we observe:

- Size of group: 2
- Within this group:
 - $B=1, C=1$, but A : changes
- Because A changes values, it is not included in the expression
- At the end, the term of this group is: **BC**
- They are not complemented because of the values of B & $C = 1$



4 – Derive Expression from K-map (con't)

C B		A	
		0	1
0	0	1	0
0	1	0	1
1	1	1	1
1	0	0	1

For this group, we observe:

- Size of group: 2
- Within this group:
 - B=1, A=1, but C: changes
- Because C changes values, it is not included in the expression
- At the end, the term of this group is: **AB**
- They are not complemented because of the values of A & B = 1



4 – Derive Expression from K-map (con't)

C B \ A		A	
		0	1
C	0	0 <td>1</td>	1
	1	1 <td>0</td>	0
	0	0	1
	1	1	1
	1	0	1

The K-map shows a group of two 1s in the column where A=1 and C=1, specifically at (C=0, B=0) and (C=1, B=1). A purple box highlights these two cells, and a purple arrow points from this group towards the text on the right.

For this group, we observe:

- Size of group: 2
- Within this group:
 - C=1, A=1, but B: changes
- Because B changes values, it is not included in the expression
- At the end, the term of this group is: **AC**
- They are not complemented because of the values of A & C = 1



4 – Derive Expression from K-map (con't)

		A	
		0	1
C	B		
	0	0	1
	1	1	0
	0	1	1

The K-map above shows four groups of 1s circled in different colors:

- A blue circle around the 1 at (C=0, B=0, A=0).
- A green circle around the 1 at (C=0, B=1, A=1).
- A red circle around the 1s at (C=1, B=0, A=0) and (C=1, B=0, A=1).
- A purple circle around the 1s at (C=1, B=1, A=0) and (C=1, B=1, A=1).

When putting it all together, we end up with an expression:

$$\text{OUT} = A'B'C + BC + AB + AC$$

....if we compare this with the traditional way... (next slide)



K - maps / SoP / PoS

- If we look back at the Random Truth Table
- We extract the terms when the output 'OUT' is **true or Sum-of-Products (SoP... on this a bit later)**

C	B	A	OUT	
0	0	0	1	→ A'B'C'
0	0	1	0	
0	1	0	0	
0	1	1	1	→ ABC'
1	0	0	0	
1	0	1	1	→ AB'C
1	1	0	1	→ A'BC
1	1	1	1	→ ABC

$$\text{OUT} = A'B'C' + ABC' + AB'C + A'BC + ABC$$

Factor out BC, Theorem 5

$$\text{OUT} = A'B'C' + ABC' + AB'C + BC$$

Theorem 11D

$$\text{OUT} = A'B'C' + ABC' + AC + BC$$

Theorem 11D

$$\text{OUT} = A'B'C' + AB + AC + BC$$

Same result as the K-map



K - m a p s / S o P / P o S

- You may say it wasn't easier or faster to do the K-map vs. Boolean
- However, if the truth table expands to 4/5/6/... input variables -> terms are a bit longer
- More input variables -> cover more outcomes
- If more outcomes are true, more product (AND) terms exists -> more Booleans steps -> more mistakes -> may not reach optimum expression

$$\text{OUT} = A'B'C' + ABC' + AB'C + A'BC + ABC$$

Factor out BC, Theorem 5

$$\text{OUT} = A'B'C' + ABC' + AB'C + BC$$

Theorem 11D

$$\text{OUT} = A'B'C' + ABC' + AC + BC$$

Theorem 11D

$$\text{OUT} = A'B'C' + AB + AC + BC$$

Same result as the K-map



- Up a level ...:::> 4-variable K-map, let's use another random truth table
- Since there are 4 variables: 2 variables for ROWS (MSBits), 2 variables for COLUMNS (LSBits)

	z	y	x	w	f
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	0
14	1	1	1	0	1
15	1	1	1	1	1

z y		x w			
		0 0	0 1	1 1	1 0
0	0	0	1	3	2
	1	4	5	7	6
1	1	12	13	15	14
	0	8	9	11	10



- Place 'f'-output values
- First 4 outcomes.....

	z	y	x	w	f
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	0
14	1	1	1	0	1
15	1	1	1	1	1

z y		x w			
		0 0	0 1	1 1	1 0
z	0 0	1 ⁰	0 ¹	0 ³	1 ²
	0 1	4	5	7	6
	1 1	12	13	15	14
	1 0	8	9	11	10



- Place 'f'-output values
- Next 4 outcomes.....

	z	y	x	w	f
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	0
14	1	1	1	0	1
15	1	1	1	1	1

z y		x w			
		0 0	0 1	1 1	1 0
z	0 0	1 ⁰ 0	0 ¹ 1	0 ³ 0	1 ² 1
	0 1	1 ⁴ 1	1 ⁵ 1	0 ⁷ 0	0 ⁶ 0
	1 1	12	13	15	14
	1 0	8	9	11	10



- Place 'f'-output values
- Next 4 outcomes.....

	z	y	x	w	f
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	0
14	1	1	1	0	1
15	1	1	1	1	1

z y		x w			
		0 0	0 1	1 1	1 0
z	0 0	1 ⁰ 0	0 ¹ 0	0 ³ 0	1 ² 1
	0 1	1 ⁴ 1	1 ⁵ 1	0 ⁷ 0	0 ⁶ 0
	1 1	12	13	15	14
	1 0	1 ⁸ 1	0 ⁹ 0	0 ¹¹ 0	1 ¹⁰ 1



- Place 'f'-output values
- Last 4 outcomes.....

	z	y	x	w	f
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	0
14	1	1	1	0	1
15	1	1	1	1	1

z y		x w			
		0 0	0 1	1 1	1 0
z	0 0	1 ⁰	0 ¹	0 ³	1 ²
	0 1	1 ⁴	1 ⁵	0 ⁷	0 ⁶
	1 1	1 ¹²	0 ¹³	1 ¹⁵	1 ¹⁴
	1 0	1 ⁸	0 ⁹	0 ¹¹	1 ¹⁰



- Let the grouping of 1's begin!!!
- Very interesting case when observing this first **1**

		x w			
		0 0	0 1	1 1	1 0
z y	0 0	1 ⁰	0 ¹	0 ³	1 ²
	0 1	1 ⁴	1 ⁵	0 ⁷	0 ⁶
	1 1	1 ¹²	0 ¹³	1 ¹⁵	1 ¹⁴
	1 0	1 ⁸	0 ⁹	0 ¹¹	1 ¹⁰

The first intent is to group this **1** with the **1s** going down the column -> max group of 4!


However, since groups exists because of the **ONE BIT OFFSET**, it also applies to the **OFFSET** that exist on the corners!

- 0->2, 0->8: 1 bit-offset
- 2->0, 2->10: 1 bit-offset
- 8->0, 8->10: 1 bit offset
- 10->8; 10->2: 1 bit offset

Ergo, they can be grouped!



- The way we group the corners:

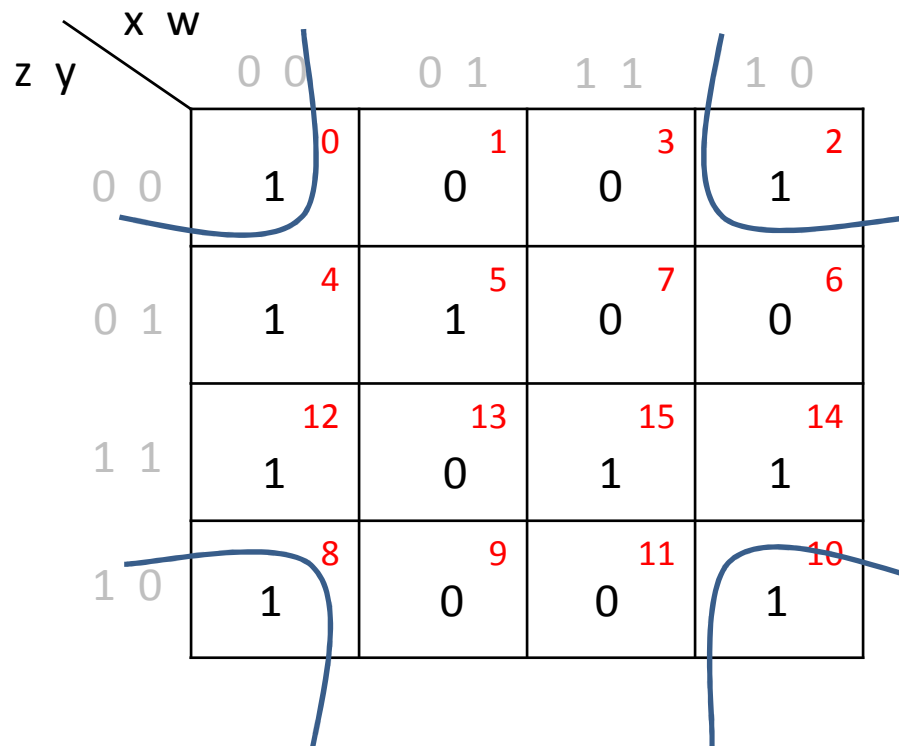


This yields to a derived term:

$$w'y'$$

....the bigger the group, less number of variables in the term



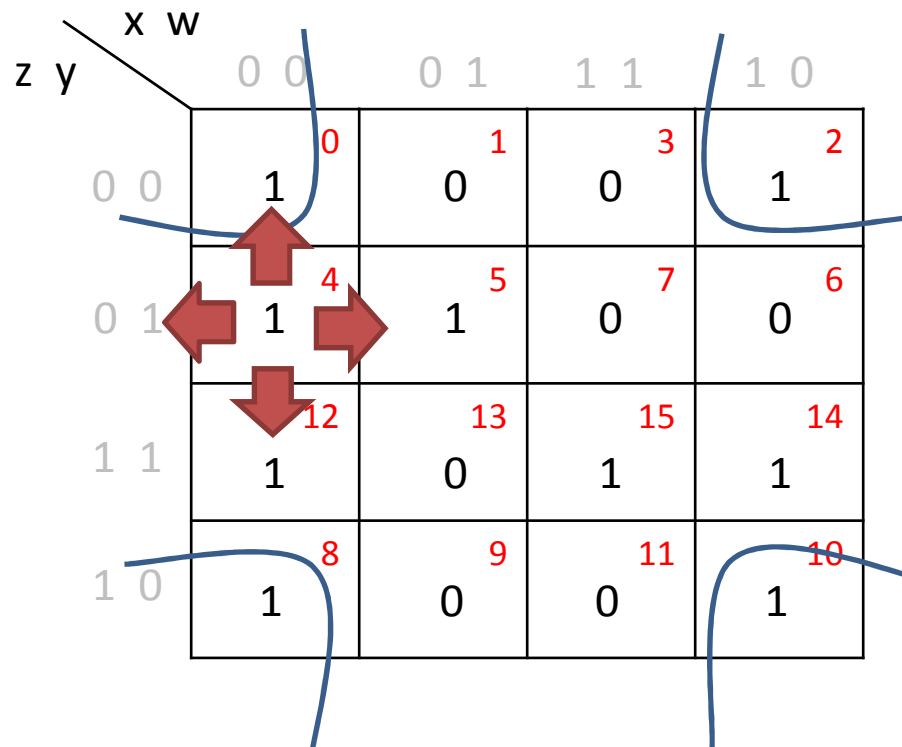
- Move to another free 1, check its neighbors, find max grouping



Since we can use 1's already part of other group(s), we can then expand the group by selecting the whole column.....

 We CAN group square 4 & 5; however, it is not the MAX size group square 4 can be part of.






The term is: $w'x'$




 - Move to another free 1, check its neighbors, find max grouping



 In this case, the max sizable group square 5 can be part of is with square 4...






Term: $x'yz'$




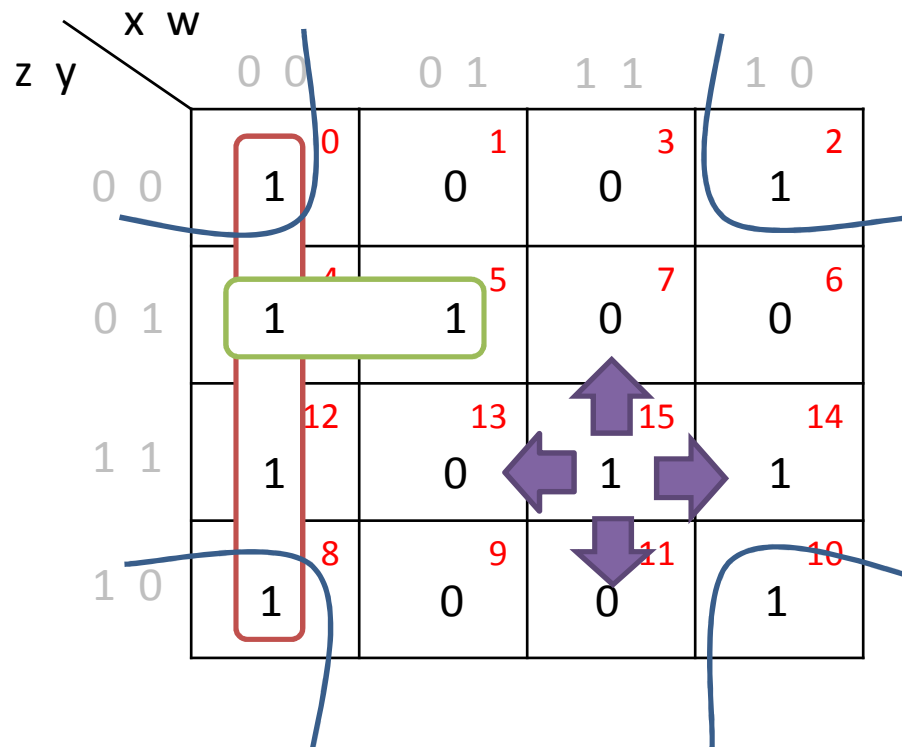- Move to another free 1, check its neighbors, find max grouping



 In this case, the max sizable group square 15 can be part of is with square 14...





Term: xyz

Final expression for 'f':

$$f = w'y' + w'x' + x'yz' + xyz$$




K - m a p s / S o P / P o S

- When using K-maps, the final expression contains terms that are **products** (ANDed-grouping of 1's) of the input variables & all terms are **summed** (OR-ed)
- The expression is known as Sum-of Products (SoP)
- SoP expressions generally have circuits that look like:
 - 1 to n - # of AND gates, with
 - 1 to i,j...p - # of inputs at each AND gates

Final expression for 'f':

$$f = w'y' + w'x' + x'yz' + xyz$$

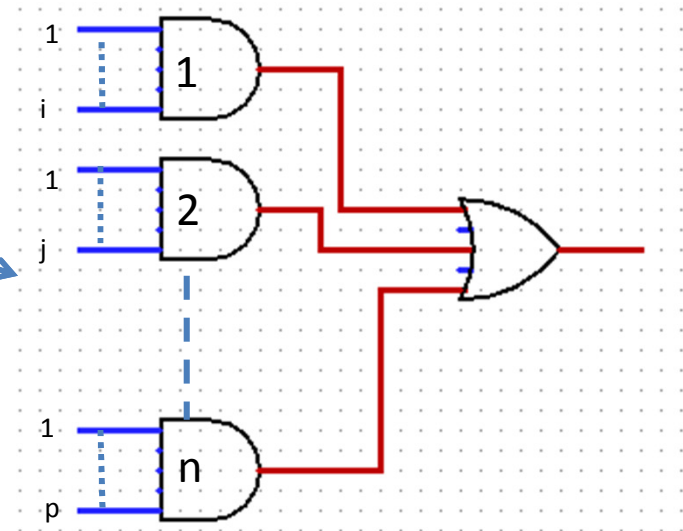

- There are times on a truth table in when....we **don't care** about the outcome
- So, the expression "don't care" came to existence to the digital design
- We mark the don't-cares with an "X" and became very useful on k-maps
- Don't-cares have a value of **either 0 or 1**....so, pick the one that is more beneficial to the design....or on the K-map!!



<http://www.viralblog.com/wp-content/uploads/2013/03/Knipsel1-500x287.jpg>



- Assume we have a system with 3 inputs -> total of 8 possible outcomes
- But, we only need the first 6 outcomes of the table for the design

Z	Y	X	OUT
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	X
1	1	1	X

- Place don't-cares (X) on the outcomes that won't matter to the truth table
- The significance of X => the outcome can be 0 or 1 (think of Schrödinger's cat without the quantum)
- Placing don't-cares on the K-map is the same as placing logical values



- K-mapping the Table.....

Z	Y	X	OUT
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	X
1	1	1	X

Z Y		X	
		0	1
0	0	1	1
0	1	0	1
1	1	X	X
1	0	0	1

- Since **don't-care** can be either 0 or 1, lets make them logical **1s**....because that's what we are grouping & want max group sizes



- K-mapping the Table.....

Z	Y	X	OUT
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	X
1	1	1	X

		X	
Z Y		0	1
0	0	1	1
0	1	0	1
1	1	X	X
1	0	0	1

$$\text{OUT} = X + Y'Z'$$

This is the variable....not the don't-care




- What happens if you group the 0's instead of the 1's?
- Same grouping rules apply
- Don't-cares can be used as 0's
- In this case:
 - Complement variables that are constant 1
 - Each term is a SUM (OR) of the variables
- You get the opposite expression:
 - Product-of-Sums (PoS)



- Example with pictures is the best way for me to stop typing...just scroll

Z	Y	X	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 


Z	Y	X	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Z Y \ X		0	1
		0 0	1
0 1	0	1	
1 1	0	0	
1 0	0	1	

$(X + Z')$




Z	Y	X	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 


$(Y' + Z')$



Z	Y	X	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

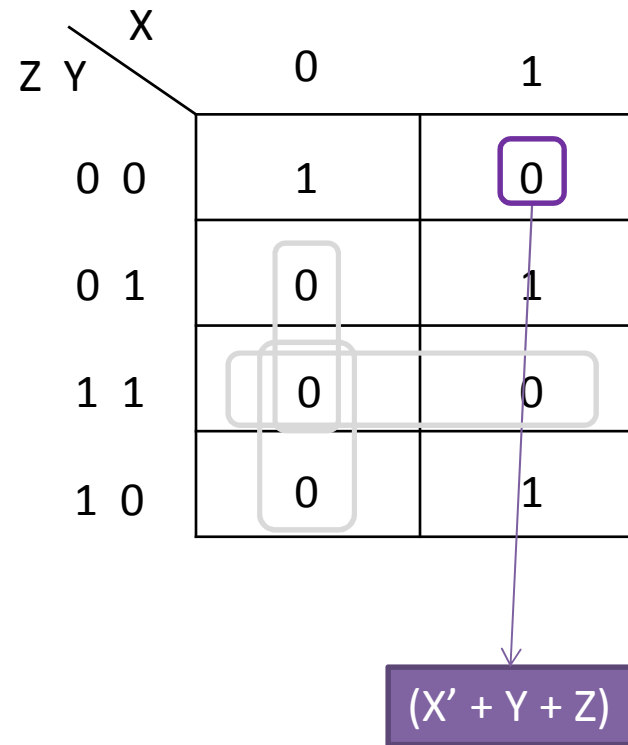

Z	Y	X	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 

$$\text{OUT} = (X + Y') \cdot (X + Z') \cdot (Y' + Z') \cdot (X' + Y + Z)$$



- Done with K-MAPS!!!..... Now go play some....

