 


From a Bubble to the next...
That's how its done

CSCI 255





http://www.edwardbosworth.com/My5155Textbook_HTM/MyText5155_Ch07_V06.htm




Sequential Circuits

  - In class, latches and flip-flops were covered
- Time is the essential part of “remembering” values
- Examples are solved on these slides




Sequential Circuits

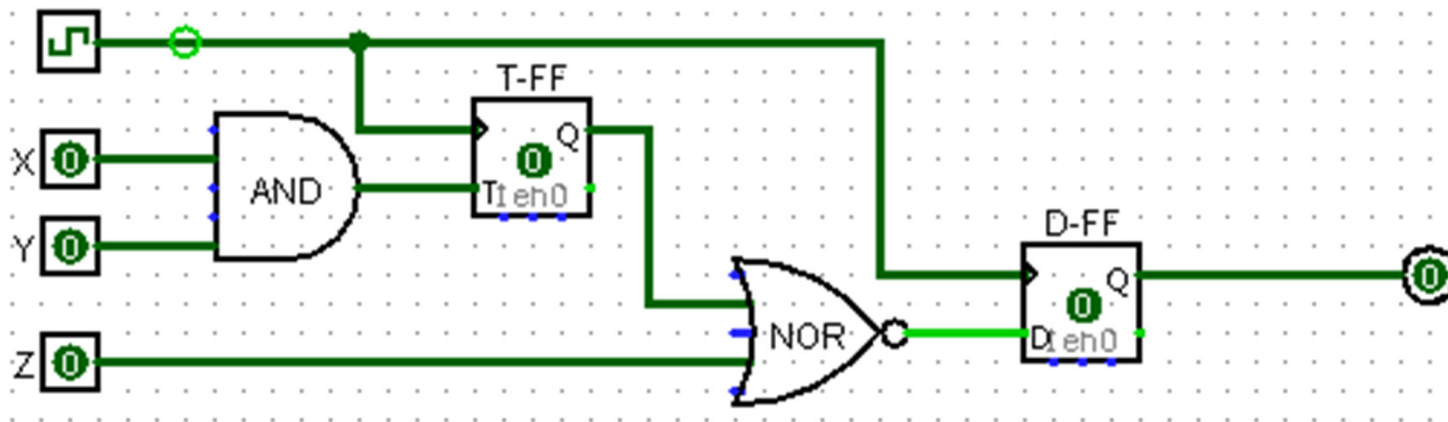
- Assume we need to time-evaluate the following circuit
- Circuit has a sequential & combinational components
- Assume all $Q_s = 0$ @ time=0
- Assume FFs are Positive-Edge triggered




Sequential Circuits

 

 
We first want to analyze the inputs of the AND gate in order to know what are the values for the T-FF. The AND gate does not depend on TIME!



Sequential Circuits

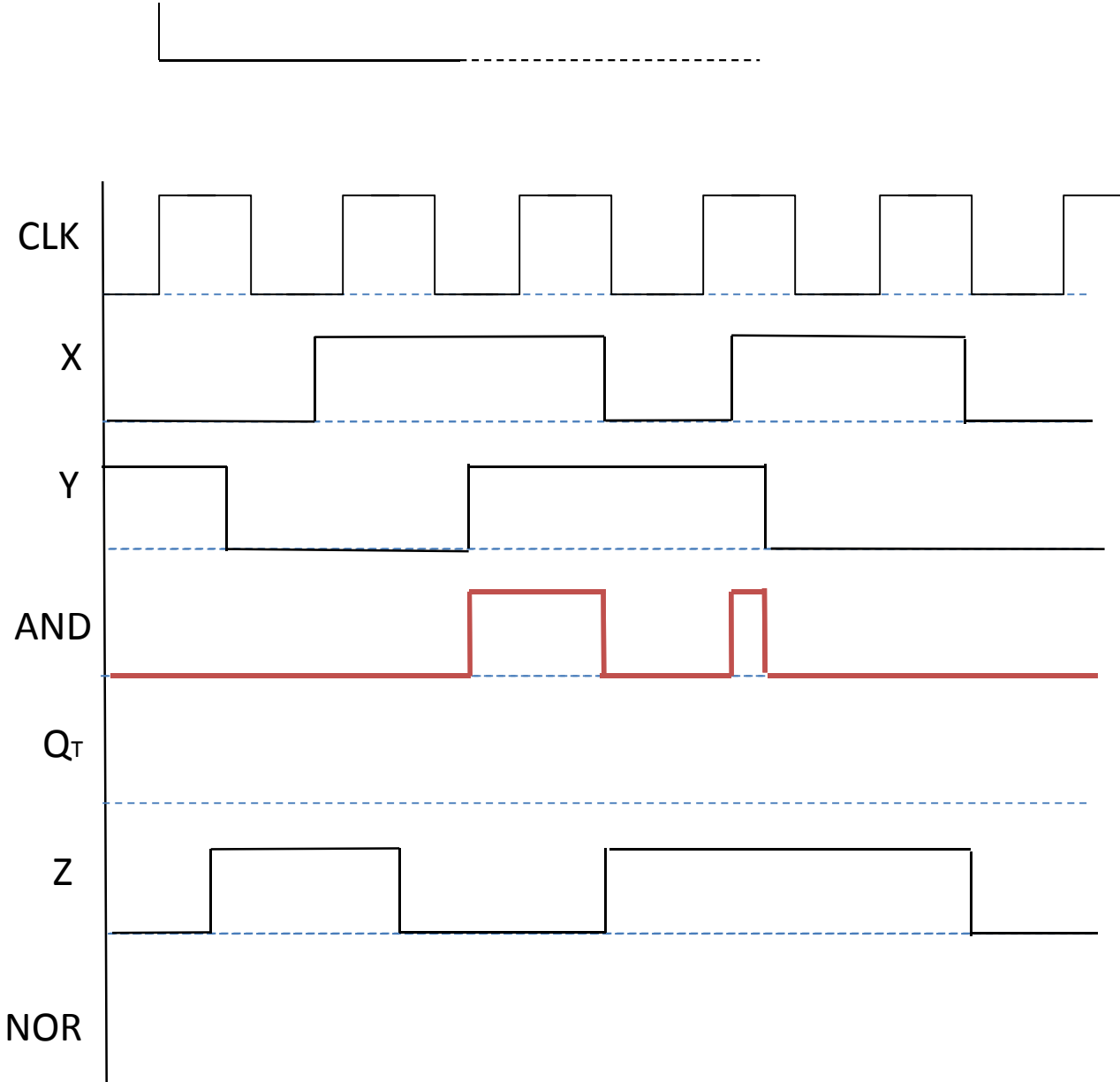


Sequential Circuits

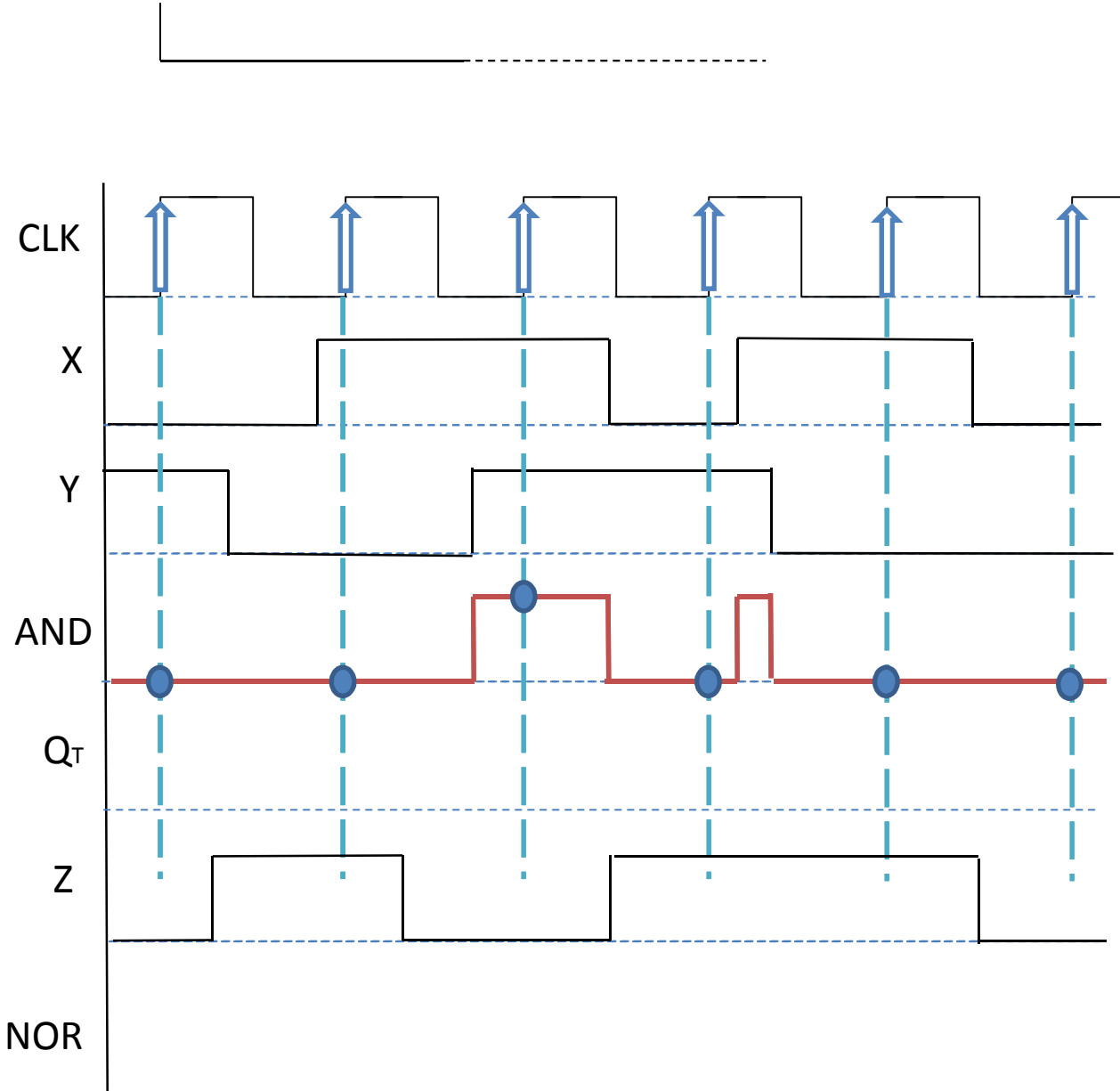

The timing result of the AND gate becomes the input signal of the T-Flip-Flop. Using the positive edge, we can then analyze Q_T . $Q=0$ @ $t=0$




Sequential Circuits

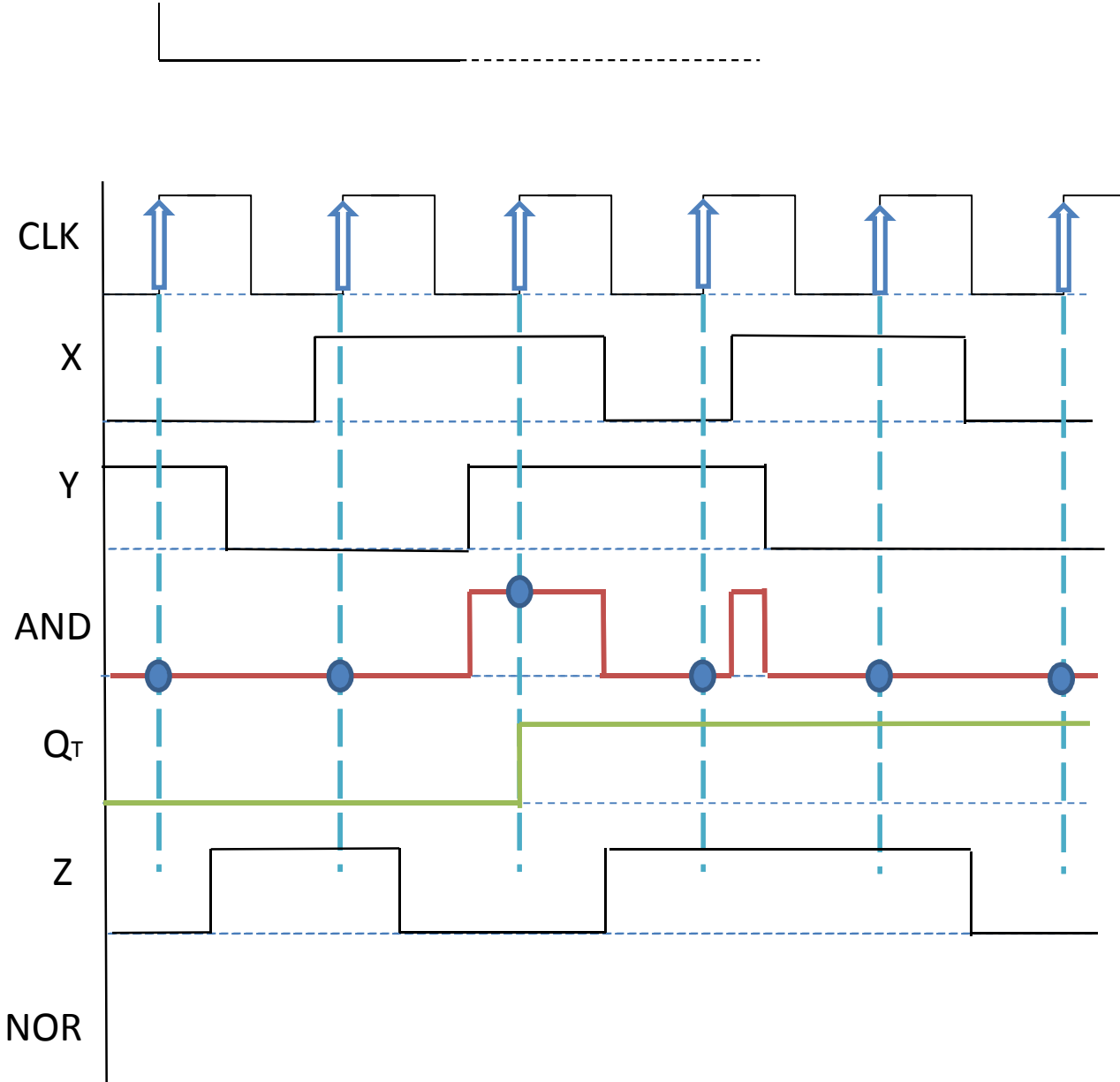

T	Q(t)	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0




Sequential Circuits

 


NOR Gate as the Z & Q_T inputs. NOR gate does not depend on the clock signal



Sequential Circuits

 


Sequential Circuits

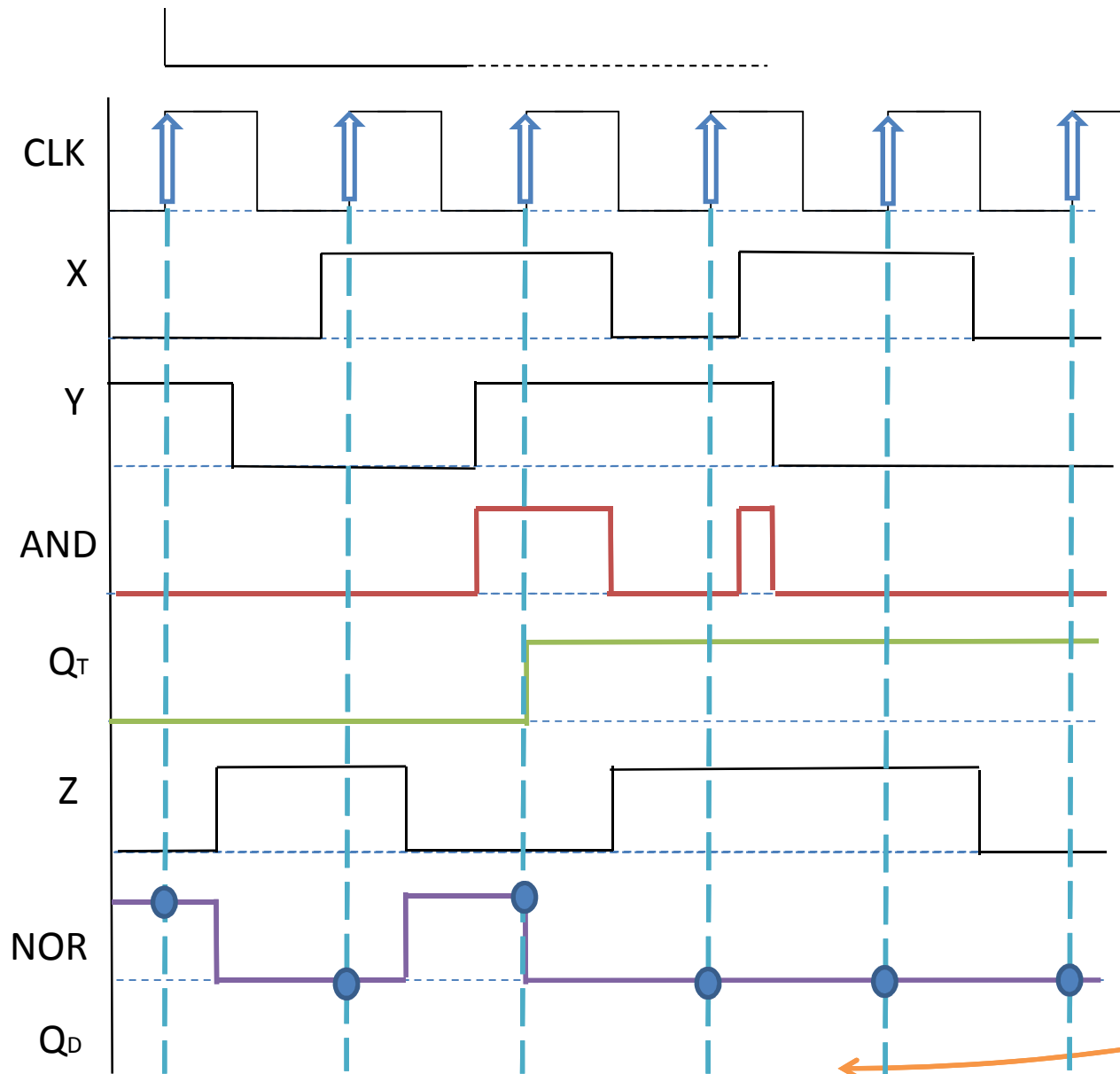


Q_D is obtained from what it reads from the D-input; which is the NOR signal in this case



Sequential Circuits

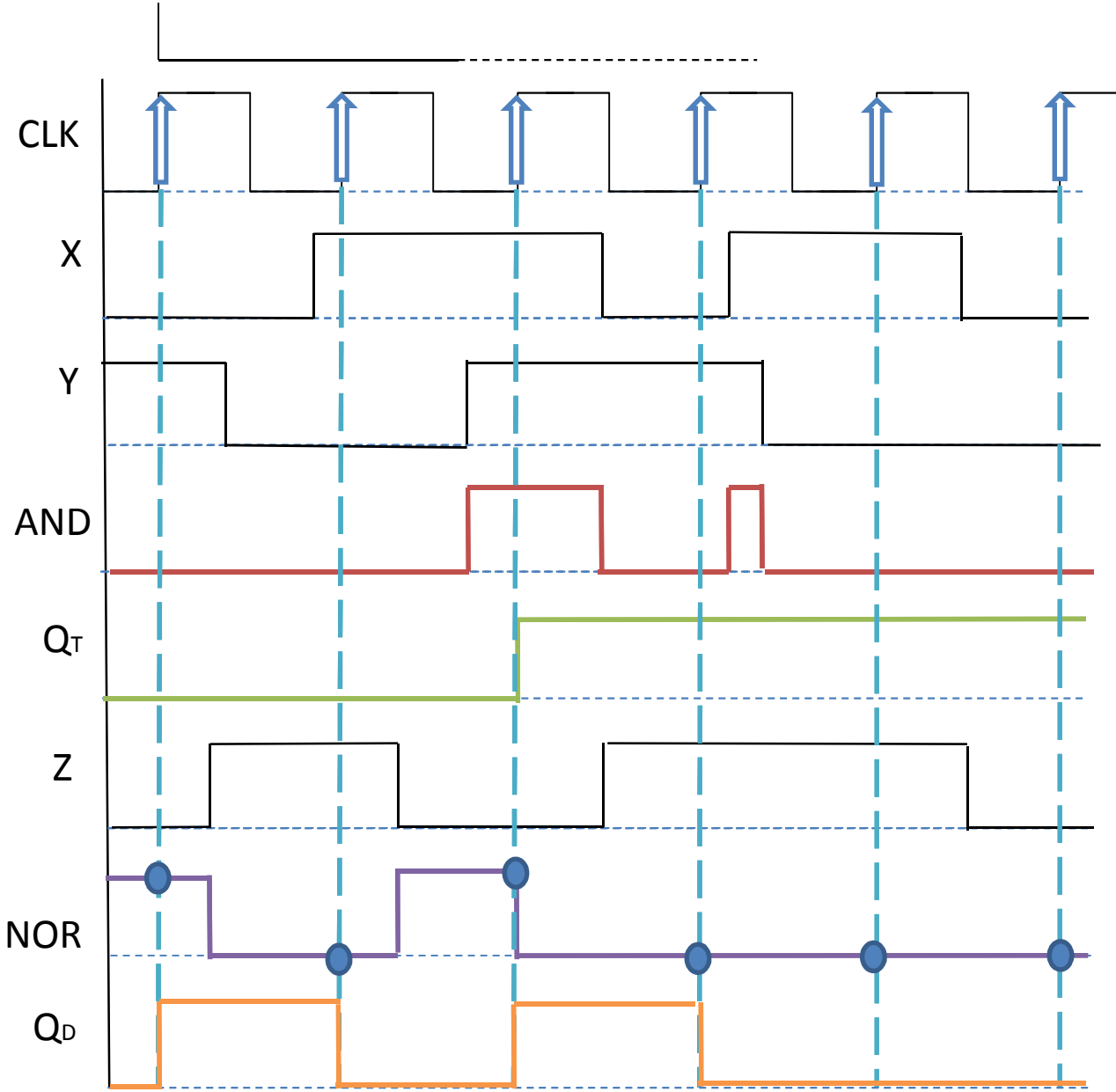

Sequential Circuits

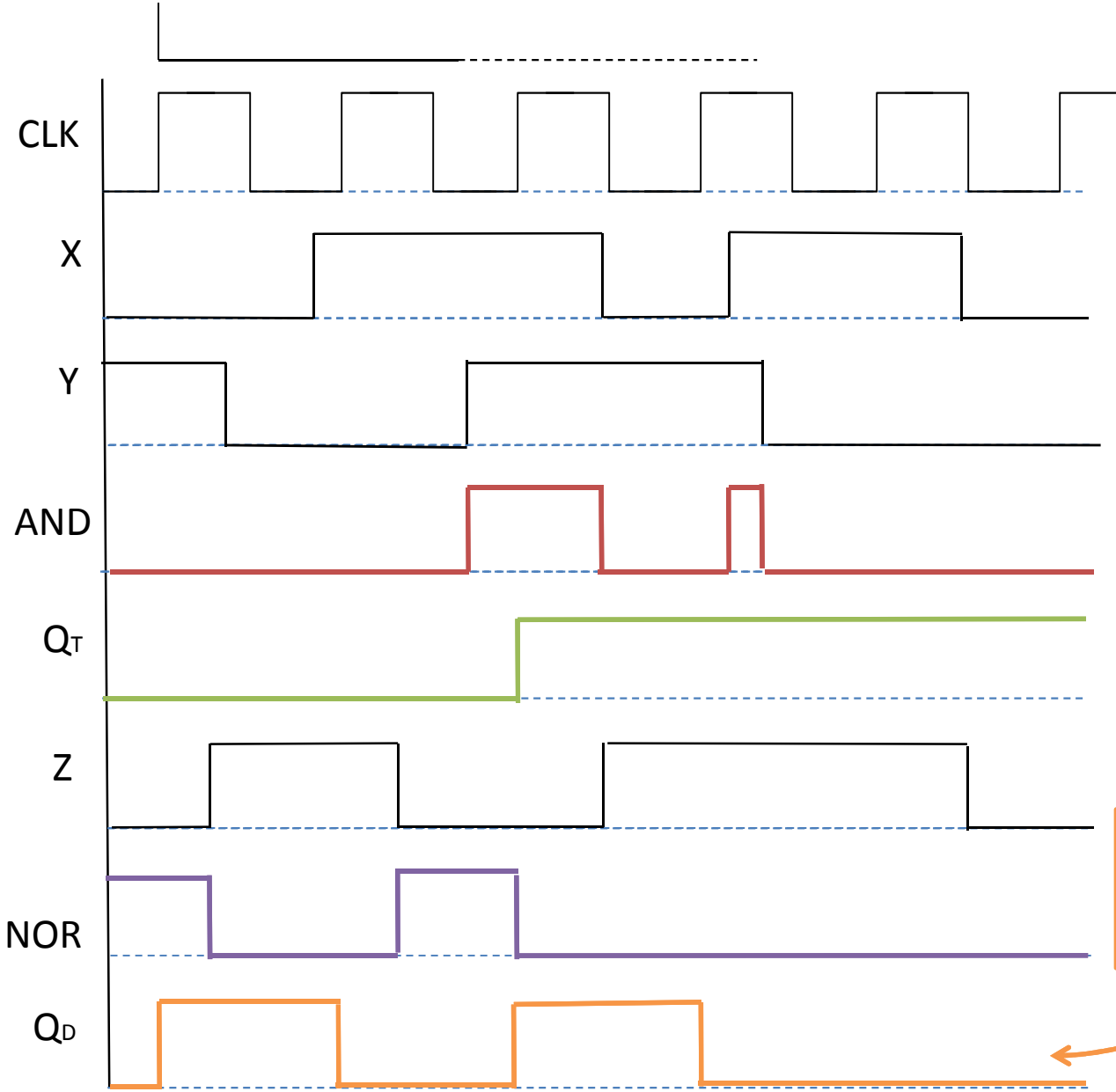


Output signal of the circuit.




Sequential Circuits

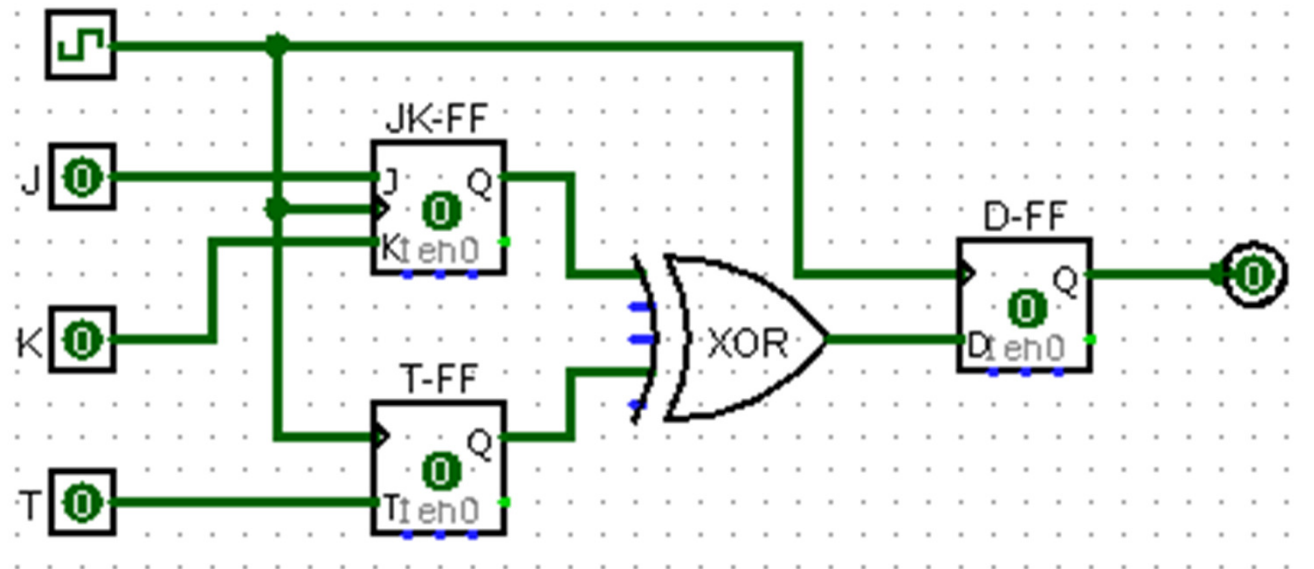- Assume we need to time-evaluate the following circuit
- Circuit has a sequential & combinational components
- Assume all $Q_s = 1$ @ time=0
- Assume FFs are Negative-Edge triggered




Sequential Circuits

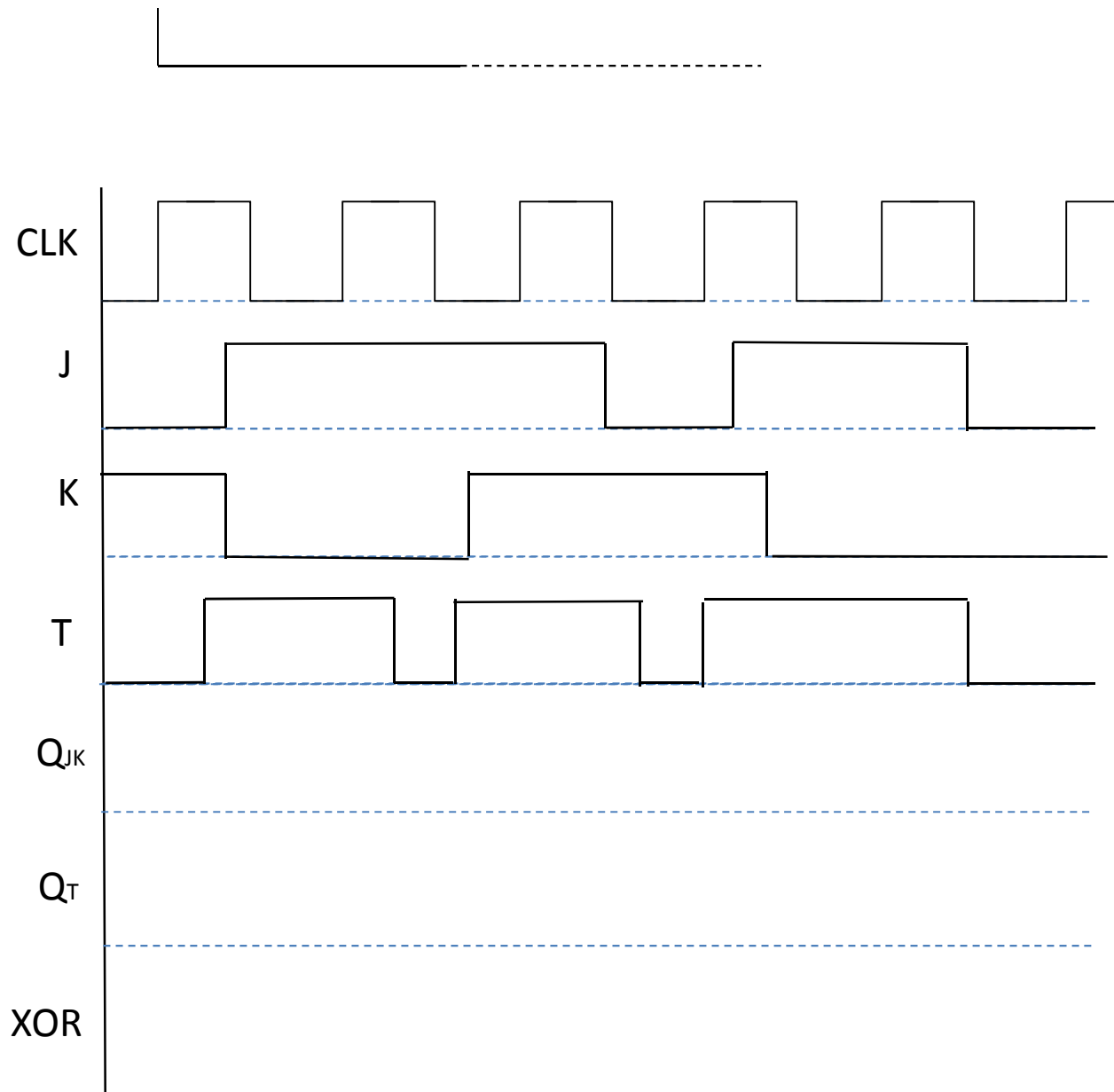

In this case, you can perform the JK & T flip flop diagrams at the same time, but to avoid mistakes.... We'll draw up JK first




Sequential Circuits

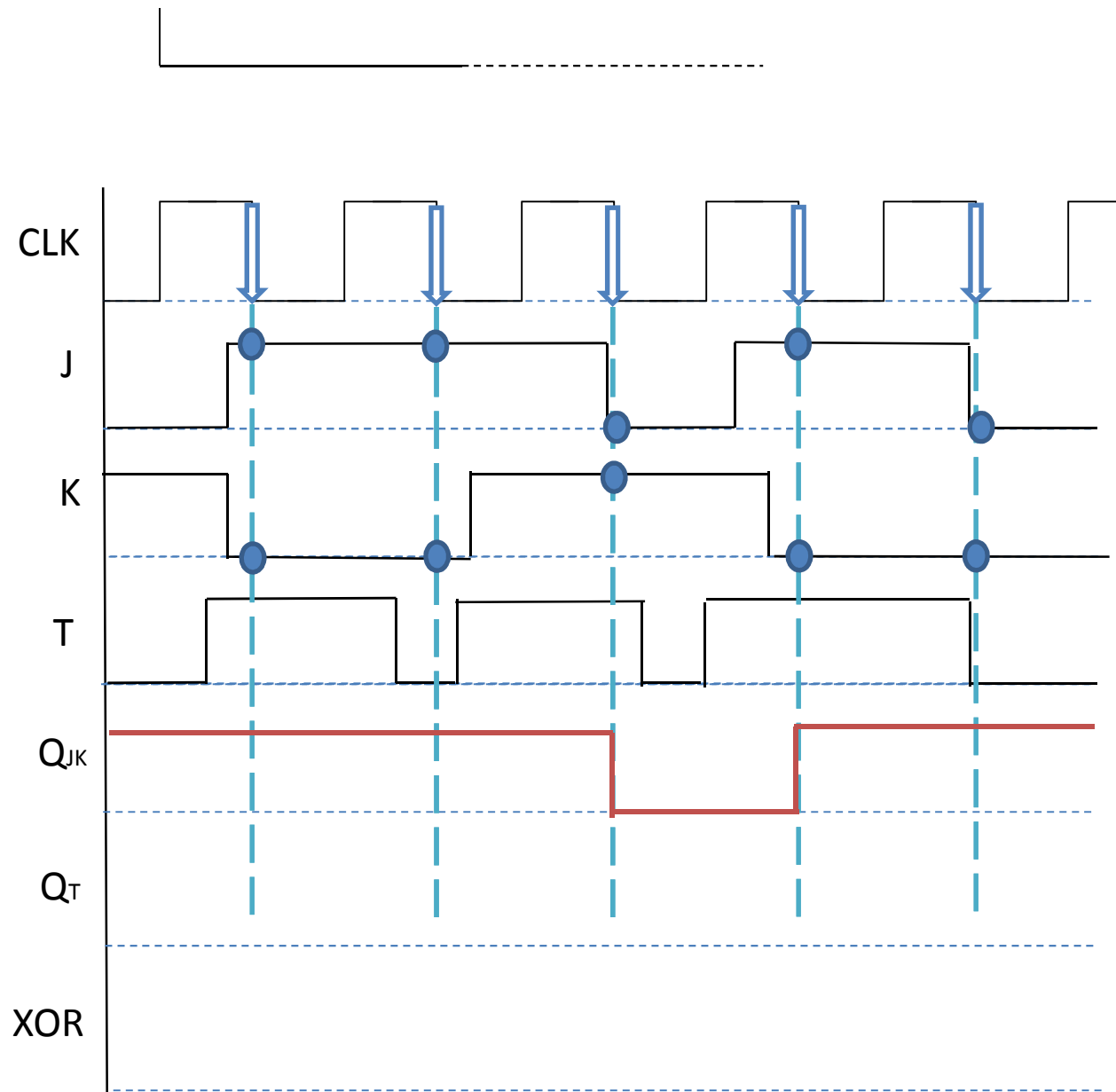

J	K	Q(t)	Q(t+1)
0	X	0	0
1	X	0	1
X	1	1	0
X	0	1	1




Sequential Circuits

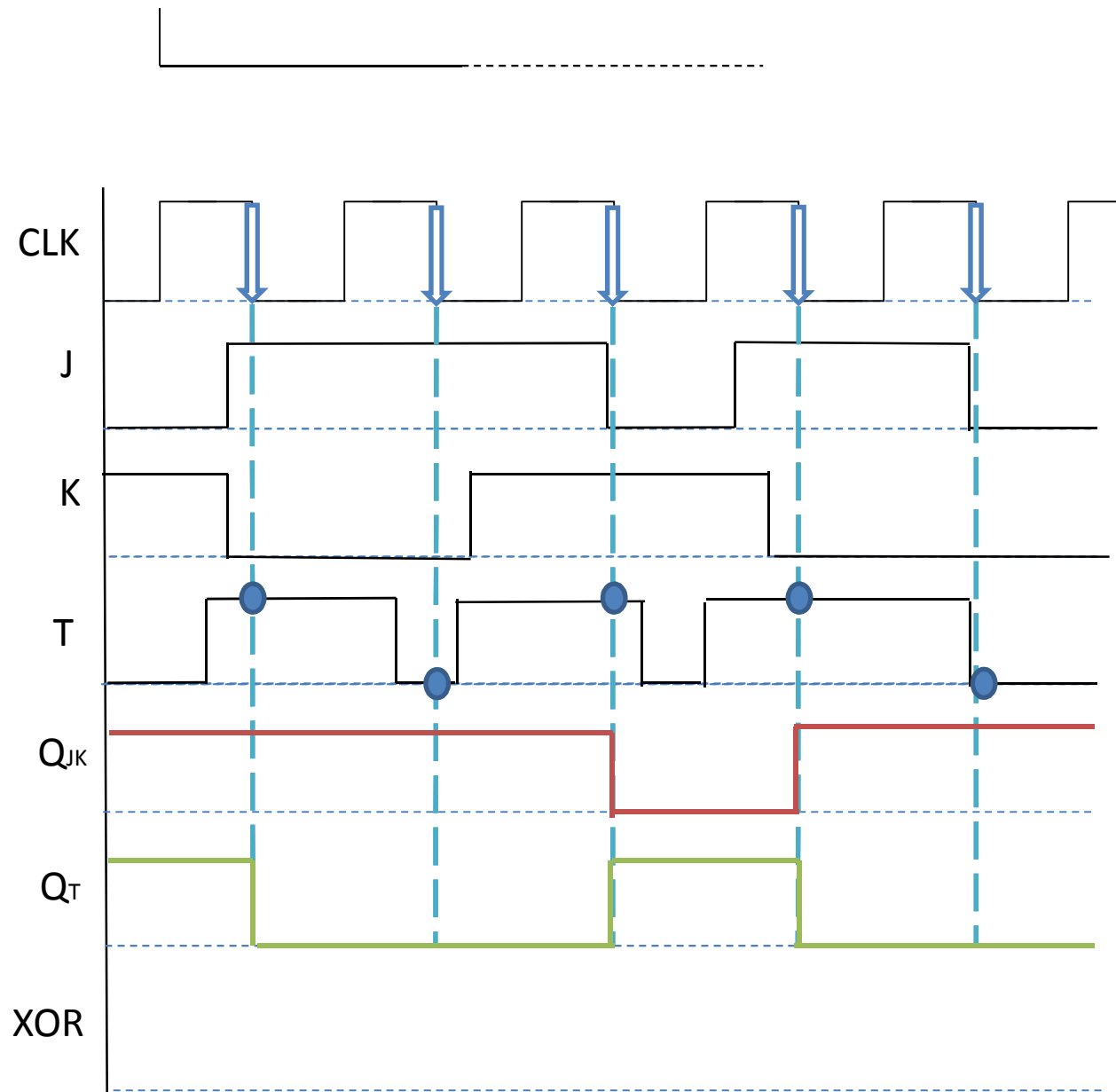

T	Q(t)	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0




Sequential Circuits

 


XOR the JK & T resulting signals. XOR does not depend on the clock signal



Sequential Circuits

 


Sequential Circuits

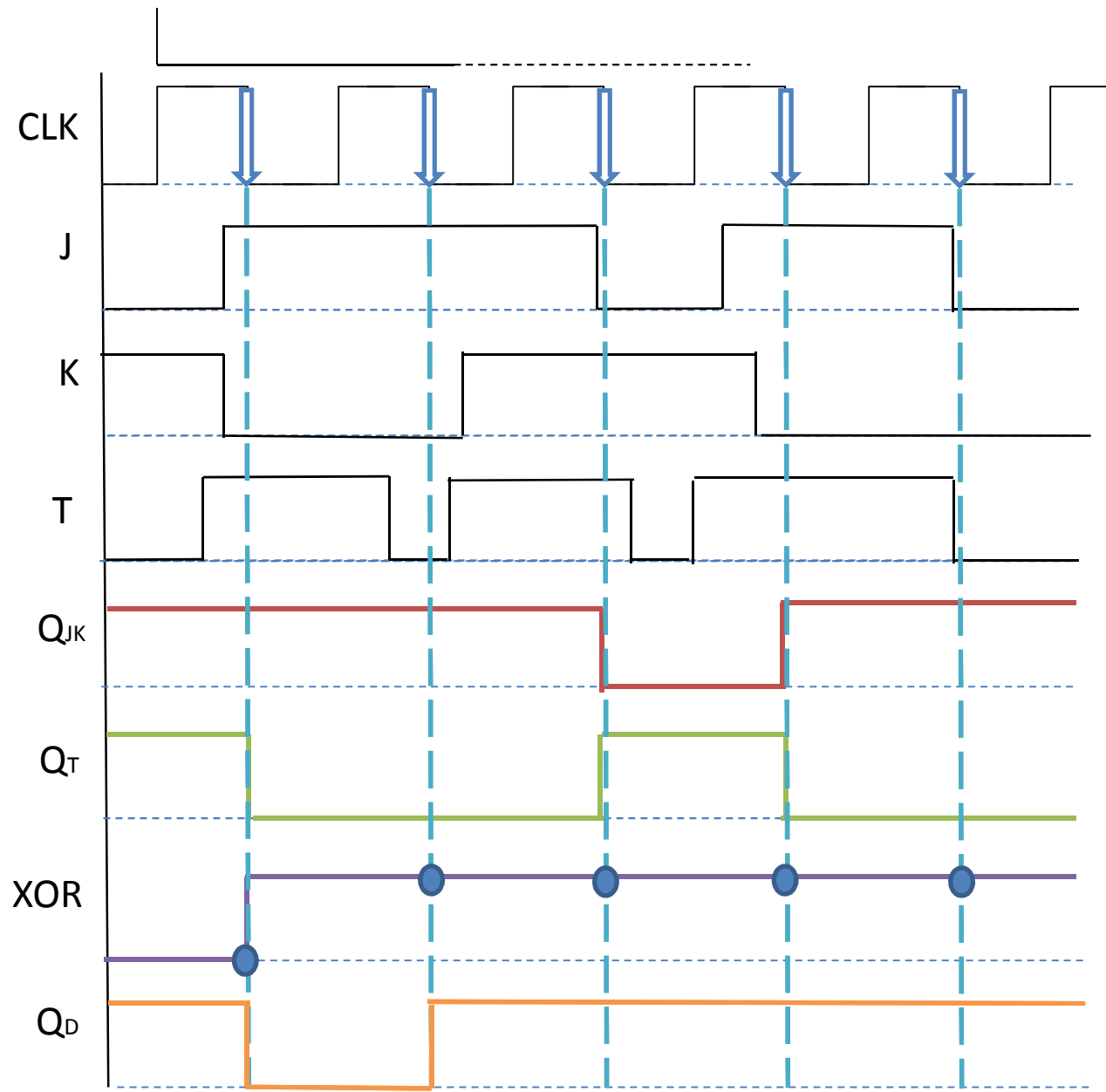

D-FF input signal is the XOR resultant signal.



Sequential Circuits

 

Output signal of the circuit

